

Chap. 6 Registers and Counters

6-1 Registers

Register : a group of FF's or a group of binary cells *FF를 모아놓은 것*
suitable for holding binary information

*n-bit register = a group of n FF's + control gates


control when and how new information
is transferred into the register

Counter : a register that goes a predetermined sequence of states upon
the application of input pulses
gates in a counter control counting sequence


module : Register를 모아놓은 것

parallel : 두개 이상
loading : 실는다


Simple example :

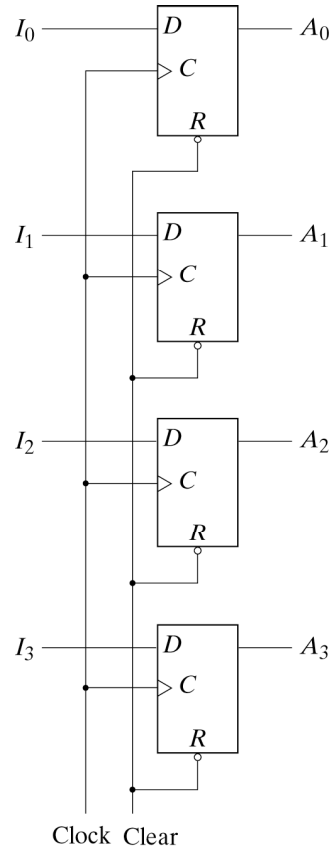

Method I

 

⇒ 동기가 개편다

 

Register with parallel load

올라가다. 전송. 적재. 실행

loading : transfer of new information into a register

parallel loading : simultaneous loading to all the bits of register with a single CP

Clock Pulse

loading control by

- master clock (CP) *Method I*
- separate control signal (CTL) to specify a particular register *Method I*

Method I

$\text{new_CP} \leftarrow \text{clk and CTL}$

gate produces t_{pd}


--> this may throw the system out of synchronism



Method II (recommended)

apply CP directly to all FF's

 and control the operation of the register with other inputs



Load high : 새로운 데이터 저장
Load low : 기존의 데이터 다시 저장

Method II example

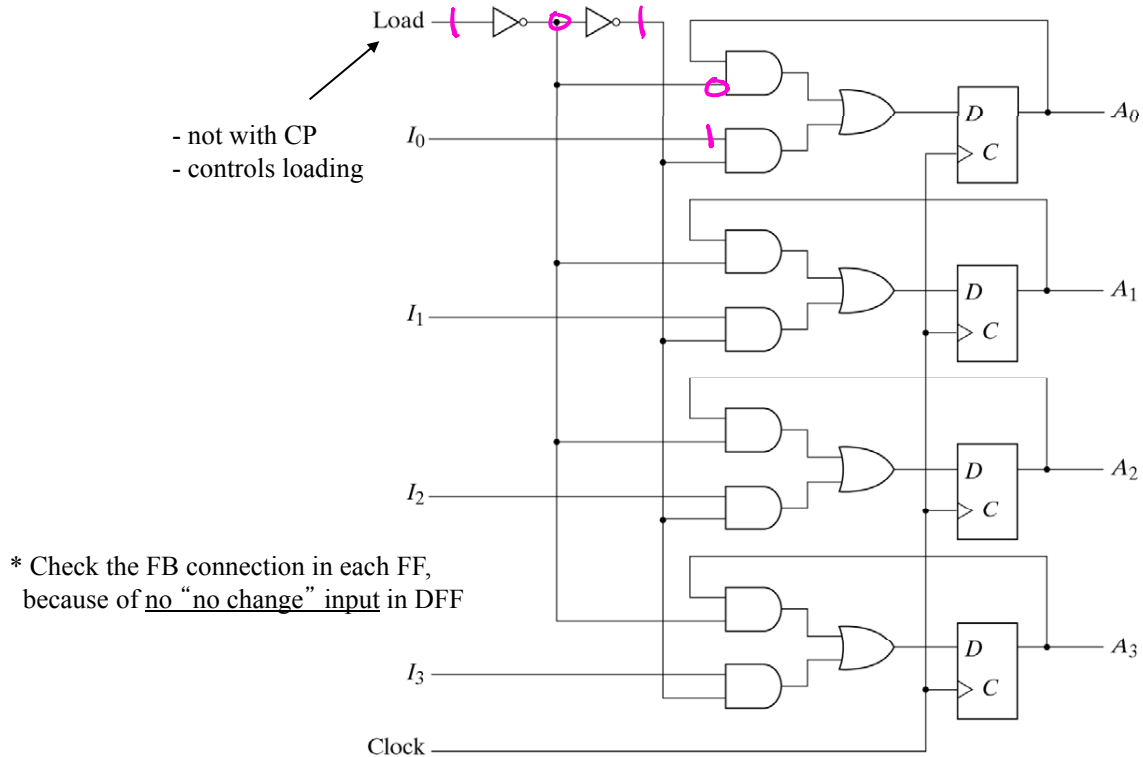


Fig. 6-2 4-Bit Register with Parallel Load

6-2 Shift Registers

: registers capable of shifting its binary information to the right or to the left.

The simplest

 


Fig. 6-3 4-Bit Shift Register


Shift right

Shift left ?

How to control shift ?


- shift only with certain pulses

method I or II of 2 pages before

 

Serial Transfer or load

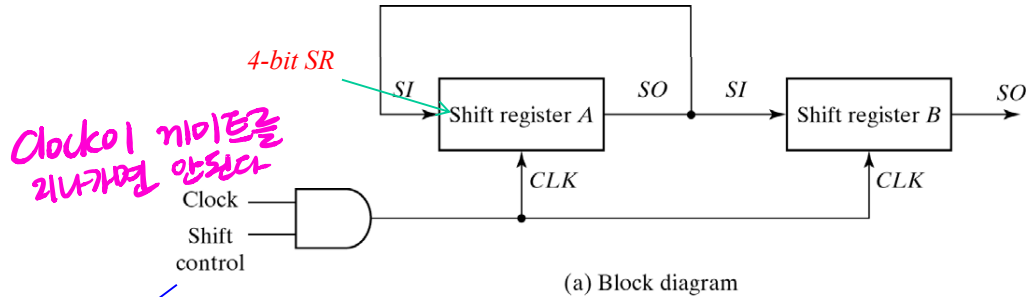In a serial mode,
information is transferred and manipulated one bit at a time



Control when and how many times

 


Fig. 6-4 Serial Transfer from Register A to register B

Table 6-1
Serial-Transfer Example

Timing Pulse	Shift Register A	Shift Register B
Initial value	1 0 1 1	0 0 1 0
After T_1	1 1 0 1	1 0 0 1
After T_2	1 1 1 0	1 1 0 0
After T_3	0 1 1 1	0 1 1 0
After T_4	1 0 1 1	1 0 1 1

Serial vs. parallel transfer

serial : one bit at a time, single input and output → less hardware

parallel : all bits at a time, several inputs and outputs → fast

Serial Adder

 


Fig. 6-5 Serial Adder

Parallel adder vs. serial adder

	parallel	serial
<i>register</i>	0 (or reg w/ p-load)	shift reg w/p-load
<i># of full adder</i>	n (for n-bits)	1
<i>carry FF</i>	0	1
<i>circuits</i>	combinational	sequential

* “reg w/ p-load” stands for “register with parallel load”

Design of serial adder using a state table

- assume that we have registers for augend and addend

- Naming:

SO from augend register x
 “ addend “ y
 FF for storing carry Q
 output; sum S

- Excitation table (If DFF is used, the result is Fig. 6-5)

Table 6-2
State Table for Serial Adder

Present State	Inputs		Next State	Output	Flip-Flop Inputs	
	x	y			J_Q	K_Q
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0

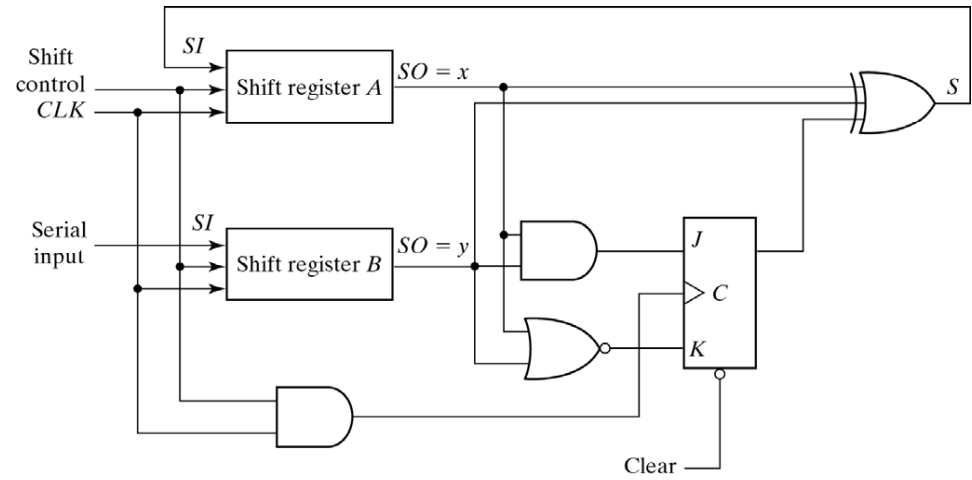
 


Fig. 6-6 Second form of Serial Adder

Universal Shift Register

Shift register with shift-left, shift-right, parallel load, parallel output capability and clear control

Operation mode selection

Table 6-3
Function Table for the Register of Fig. 6-7

Mode Control		Register Operation
s_1	s_0	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

HDL coding HW

 


Fig. 6-7 4-Bit Universal Shift Register


6-3 Ripple Counter

: register that goes through a prescribed sequence of states


ripple counter -- uses FF output as trigger signal for the next FF
synchronous counter

Binary ripple counter

Signal propagates in ripple fashion

 

(a) With T flip-flops

 

(b) With D flip-flops

Fig. 6-8 4-Bit Binary Ripple Counter

BCD ripple counter

decade counter

 


Fig. 6-9 State Diagram of a Decimal BCD-Counter

Timing diagram ?

 
 


Fig. 6-10 BCD Ripple Counter


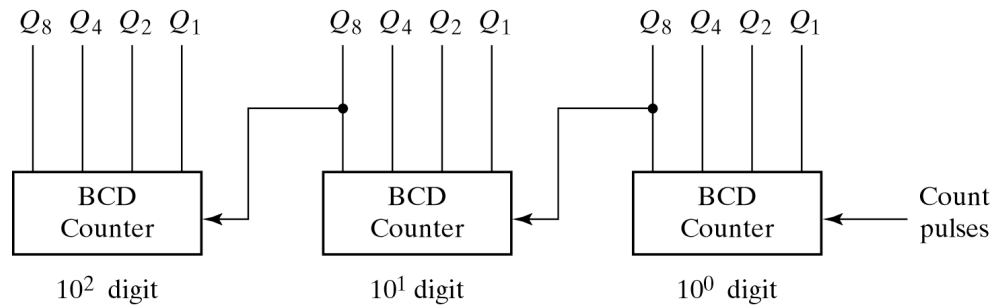


Fig. 6-11 Block Diagram of a Three-Decade Decimal BCD Counter

6-4 Synchronous Counters

 


Binary counter

A ₄	A ₃	A ₂	A ₁
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
.....			
1	1	1	1
0	0	0	0


count up ↓

count down ↑

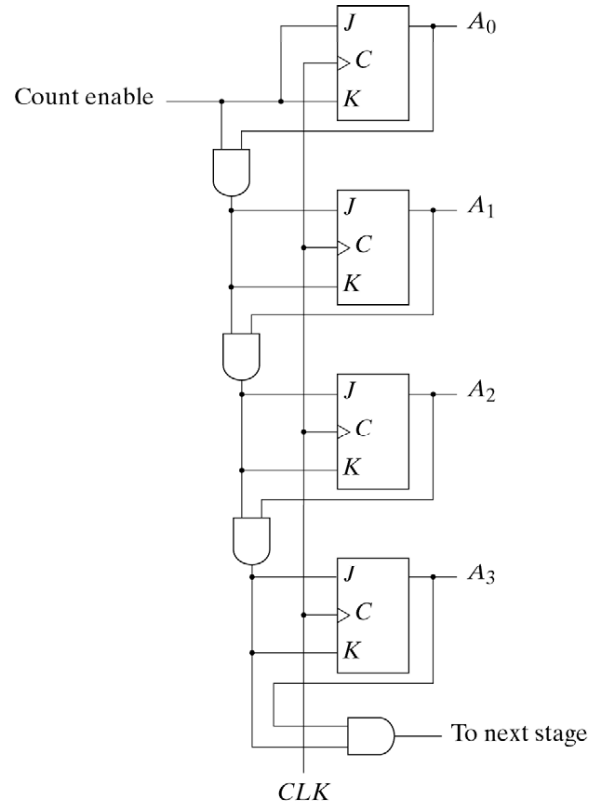

74160
161
163
164
168
169

Fig. 6-12 4-Bit Synchronous Binary Counter

 

Up counting

LSB toggles with every pulse

The others toggle when all the bits in the lower order positions='1'

Down counting

LSB toggles with every pulse

The others toggle when all the bits in the lower order positions='0'

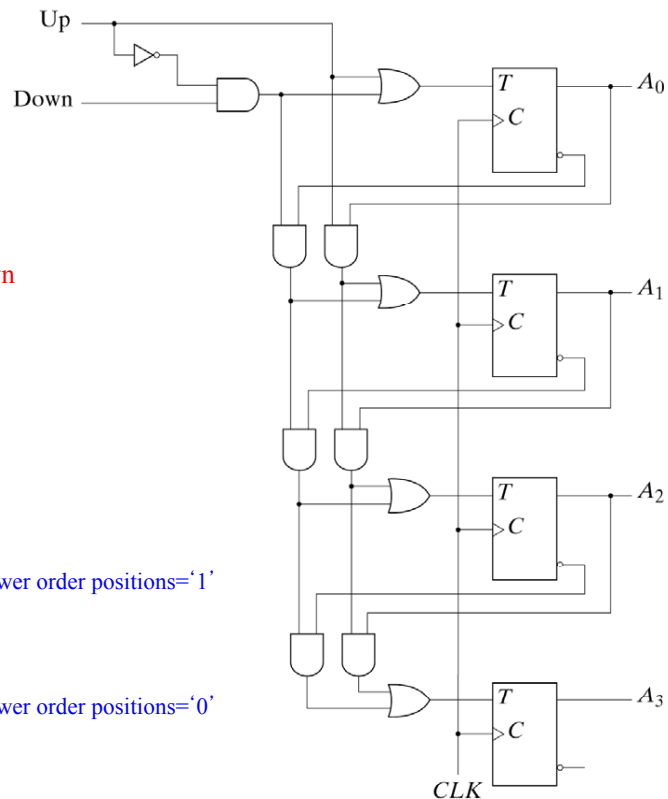



Fig. 6-13 4-Bit Up-Down Binary Counter

count up or count down

positive edge triggered 4-bits counter
with asynchronous reset
and synch load
with count controlled input

Table 6-6
Function Table for the Counter of Fig. 6-14

Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

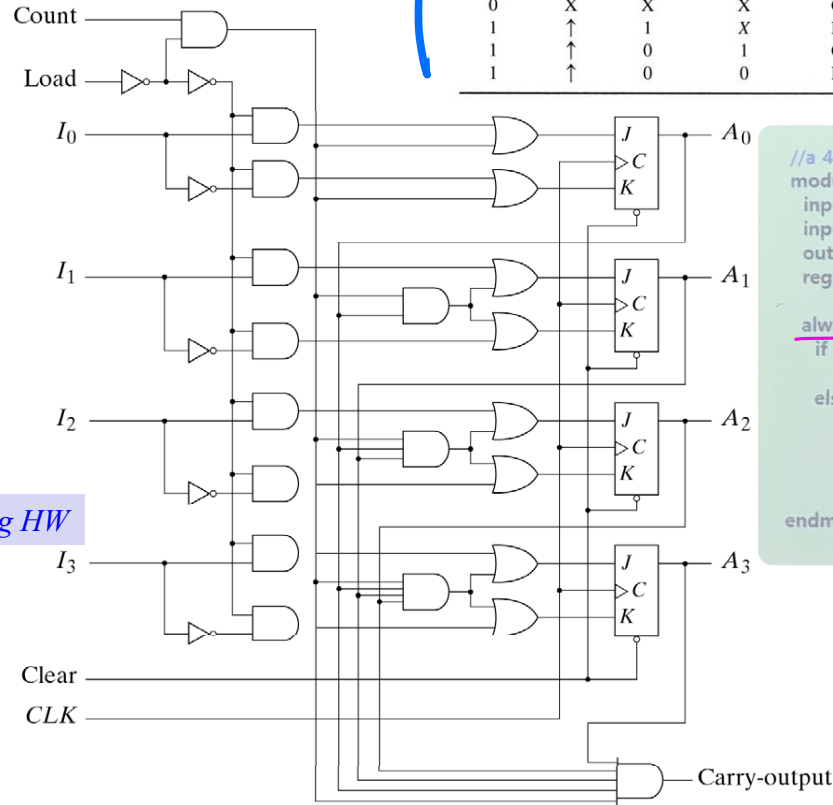

HDL coding HW

```
//a 4-bit counter w/asynch reset
module count4 (Clk, Clrn, Load, I, Q);
input Clk, Clrn, Load;
input [3:0] I;
output [3:0] Q;
reg [3:0] Q;
```

always @(posedge Clk or negedge Clrn)

if (Clrn == 0)

Q <= 0;

else

if (Load)

Q <= I;

else

Q <= Q + 1;

endmodule

BCD counters with the one in Fig. 6-14

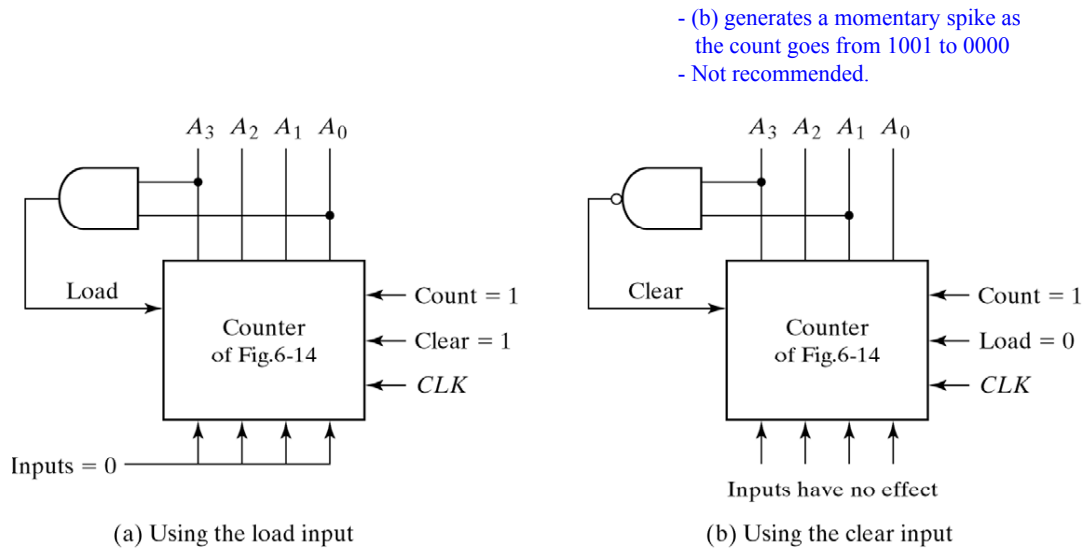


Fig. 6-15 Two ways to Achieve a BCD Counter Using a Counter with Parallel Load

6-5 Other Counters

Modulo-N counter (divide-by-N counter)

a counter that goes through a repeated sequence of N states

Applications

- counting
- used to generate timing signals for digital systems

Counter with unused states








- may treat them as “*don ’t care*” or assign specific next states
- need to check whether it eventually goes into one of the valid states


Design Example (counter with unused states)

Table 6-7
State Table for Counter


Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

       HW 3, 2, 5, 1, 0, 7, 3, ...의 순서를
반복하는 counter를 설계하라



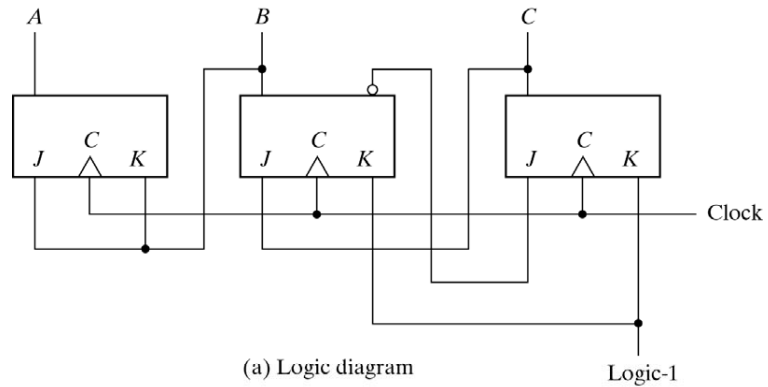

Next states for unused states ?

 

Self-correcting counter



(b) State diagram

Fig. 6-16 Counter with Unused States

Timing signals

How to transfer 32 bits data
over 8 bits bus ?

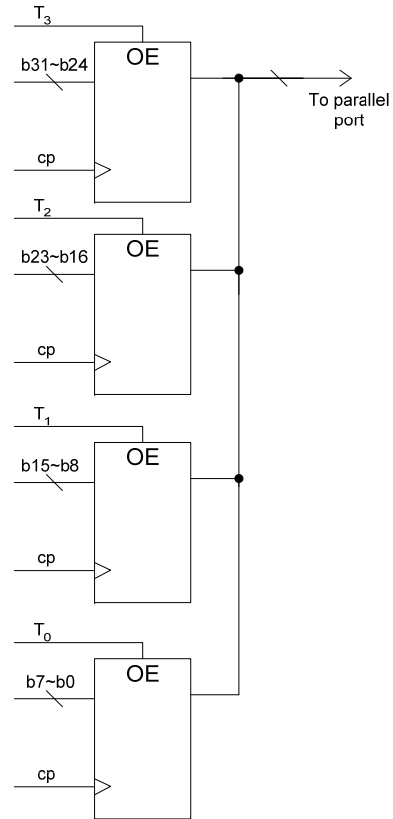 Requires timing signals that make one
enable at a time



Tristate buffer


 


FIGURE 4-29 a Three-State Buffer

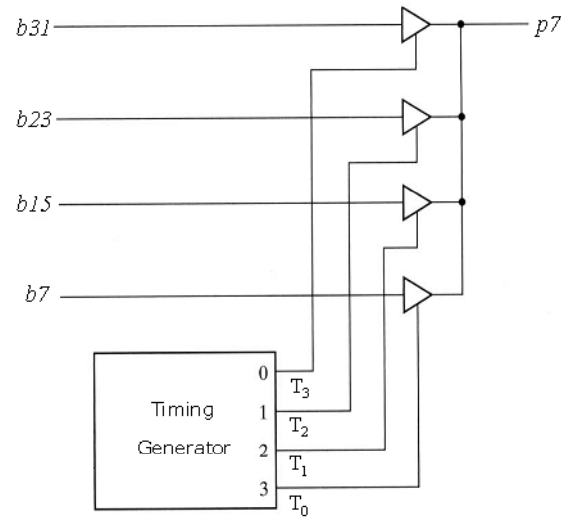HW: Tristate buffer 대신 OR 또는 AND gate 를 사용하려면?



Multiplexers with Three-State Gates

Ring Counter


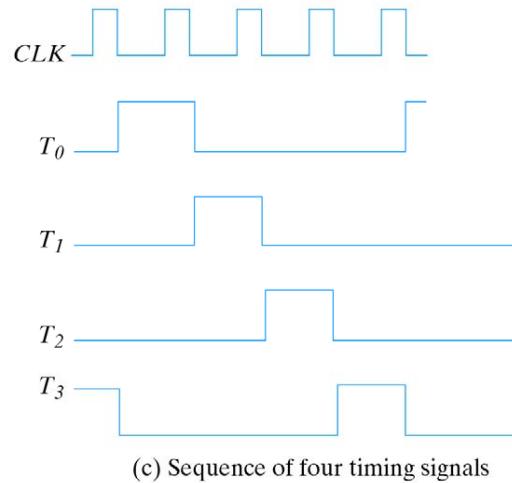
 
 


Fig. 6-17 Generation of Timing Signals

Johnson Counter

; useful in generating timing signals ($2n$ distinguishable states with n FF's)

switch-tail ring counter

 

(a) Four-stage switch-tail ring counter

Disadvantage?

How to solve?

read textbook

Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	AB'
3	1	1	0	0	BC'
4	1	1	1	0	CE'
5	1	1	1	1	AE
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

(b) Count sequence and required decoding

Fig. 6-18 Construction of a Johnson Counter

Comparison

Assume that 2^n timing signals

1. Ring counter

2^n FF's

2. Counter and decoder

n bit counter and n-to 2^n decoder (2^n n-input AND gates)


3. Johnson counter and decoder

$2^{(n-1)}$ FF's + 2^n 2-input AND gates

disadvantage : once it gets into an unused state, it will stay out of used states

How to solve? $D_C = (A+C)B$

6-6 HDL codes

 

Function Table 만들기.

+ Quartus
waveform

4 4 4 4

```
//HDL Example 6-1
//-----
//Behavioral description of Universal shift register
// Fig. 6-7 and Table 6-3
module shftreg (s1,s0,Pin,lfin,rtin,A,CLK,Clr);
    input s1,s0;           //Select inputs
    input lfin, rtin;       //Serial inputs
    input CLK,Clr;         //Clock and Clear
    input [3:0] Pin;       //Parallel input
    output [3:0] A;        //Register output
    reg [3:0] A;
    always @ (posedge CLK or negedge Clr)
        if (~Clr) A = 4'b0000;
        else
            case ({s1,s0})
                2'b00: A = A;           //No change
                2'b01: A = {rtin,A[3:1]}; //Shift right
                2'b10: A = {A[2:0],lfin}; //Shift left
                2'b11: A = Pin;         //Parallel load input
            endcase
endmodule
```

이거 빼면 동작 Clr

```
//HDL Example 6-3
//-----
//Binary counter with parallel load
//See Figure 6-14 and Table 6-6
module counter (Count,Load,IN,CLK,Clr,A,CO);
    input Count,Load,CLK,Clr;
    input [3:0] IN;           //Data input
    output CO;               //Output carry
    output [3:0] A;          //Data output
    reg [3:0] A;
    assign CO = Count & ~Load & (A == 4'b1111);
    always @ (posedge CLK or negedge Clr)
        if (~Clr) A = 4'b0000;
        else if (Load) A = IN;
        else if (Count) A = A + 1'b1;
        else A = A;           // no change, default condition
endmodule
```