

State graphs

Constraints on Input Labels for Every State S_k

1. If I_i and I_j are any pair of input labels on arcs exiting state S_k , then $I_i I_j = 0$ if $i \neq j$.
2. If n arcs exit state S_k and the n arcs have input labels I_1, I_2, \dots, I_n , respectively, then $I_1 + I_2 + \dots + I_n = 1$.


Notations for state graphs

$X_i X_j / Z_p Z_q$


In case of

4 inputs (X_1, X_2, X_3, X_4)
and 4 outputs (Z_1, Z_2, Z_3, Z_4)

 $X_1 X_4' / Z_2 Z_3$
means 1 - - 0 / 0110


 
$$\begin{aligned}
 (X_1)(X_1'X_2') &= 0 \\
 (X_1)(X_1'X_2) &= 0 \\
 (X_1'X_2')(X_1'X_2) &= 0 \\
 X_1 + X_1'X_2' + X_1'X_2 &= 1
 \end{aligned}$$



Inputs are $X_1 X_2 X_3$
($X_1 = X_2 = 1$ not allowed)

	000	001	010	011	100	101	110	111
S_k	S_k	S_k	S_q	S_q	S_p	S_p	-	-

1. state table

shows what the output is and what the next state is, for each input combination and each state.

2. state diagram (or state graph)

a graphical representation of the system behavior, showing for each input combination and each state what the output is and what the next state is

Table 6.1 A state table.

Present state	Next state		Output
	$x = 0$	$x = 1$	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

Notation


the present state q

the next state q^* , $q†$, $q(t+\Delta)$

Next state?

what will be stored in memory after this clock transition

Figure 6.3 A state diagram.

 


Timing trace for the Table 6.1

Table 6.1 A state table.

Present state	Next state		Output
	$x = 0$	$x = 1$	
<i>A</i>	<i>A</i>	<i>B</i>	0
<i>B</i>	<i>A</i>	<i>C</i>	0
<i>C</i>	<i>A</i>	<i>D</i>	0
<i>D</i>	<i>A</i>	<i>D</i>	1

Figure 6.3 A state diagram.

 

Trace 6.2 Trace with state

x	0	1	1	0	1	1	1	0	0	1	0	1	1	1	1	1	0	0		
q	?	A	B	C	A	B	C	D	A	A	B	A	B	C	D	D	D	A	A	?
z	?	0	0	0	0	0	0	1	0	0	0	0	0	0	1	1	1	0	0	0

Terminology once more

State: 메모리에 저장되어 있는 2진수 값.


State table: PS와 각 입력조합에 대하여 출력과 NS를 나타낸 도표
(NS: 다음 클럭 후 메모리에 저장될 값)

State diagram or state graph: 상태표를 그림으로 나타낸 것.

Table 5.1 A sample state table.

q	q*		z	
	x = 0	x = 1	x = 0	x = 1
A	A	B	0	0
B	C	B	1	0
C	A	D	0	0
D	C	C	0	0

Figure 5.3 A state diagram.

 


Sequential system is often called as *state machine* or *finite state machine(FSM)*

Flip-flop

- D, JK, SR, T
- clocked binary storage device
- rising (leading)-edge triggered or falling (or trailing)-edge triggered

Figure 5.6 Trailing-edge triggered flip flop timing.

 

D Flip-flop

Figure 6.7 D flip-flop diagrams.



 


Figure 6.8 D flip flop state diagram.

 


Timing diagram of DFF

Figure 6.9 *D* flip flop timing diagram.

 

(a)

 

Preset and clear

Figure 6.13 Flip flop with clear and preset inputs.


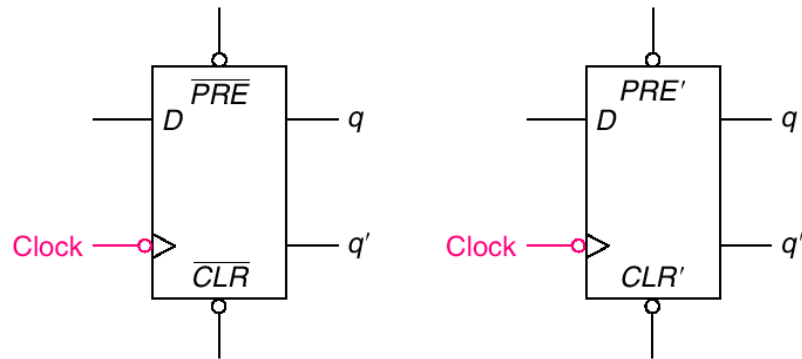


Table 6.3 D flip flop with clear and preset inputs behavioral table.

$\overline{PRE'}$	$\overline{CLR'}$	D	q	q^*
0	1	X	X	1
1	0	X	X	0
0	0	X	X	—
<hr/>				
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

Figure 6.14 Time for flip flop with clear and preset.

 

S/RFF

Figure 6.15 SR flip flop state diagram.


 


Figure 6.16 SR flip flop timing diagram.

 

TFF

Figure 6.17 T flip flop state diagram.


 


Figure 6.18 T flip flop timing diagram.

 

J/K FF

Figure 6.19 JK flip flop state diagram.


 


Figure 6.20 Timing diagram for JK flip flop.

 

Analysis of sequential systems

From state machine to state table or state diagram

Figure 6.21 A D flip flop **Moore** model circuit.

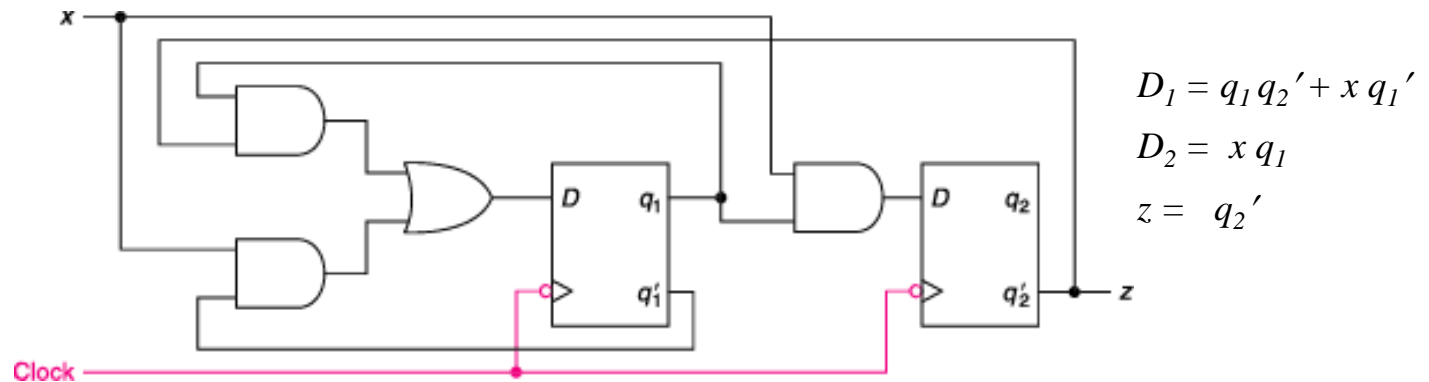


Table 6.7a Partial state table

$q_1 q_2$	$q_1^* q_2^*$		z
	$x = 0$	$x = 1$	
0 0	0	1	1
0 1	0	1	0
1 0	1	1	1
1 1	0	0	0

Table 6.7b Complete state table

$q_1 q_2$	$q_1^* q_2^*$		z
	$x = 0$	$x = 1$	
0 0	0 0	1 0	1
0 1	0 0	1 0	0
1 0	1 0	1 1	1
1 1	0 0	0 1	0


 


Figure 6.22 A Moore state diagram.

Figure 6.23 A Moore model circuit.

 

Outline of state table.

$A \ B$	$A^* B^*$		z
	$x = 0$	$x = 1$	
0 0			0
0 1			1
1 0			1
1 1			1

Table 6.8a State table with first two entries.

A B	A* B*		z
	x = 0	x = 1	
0 0	0 1		0
0 1	0 0		1
1 0			1
1 1			1

$$AB=00, x=0 \rightarrow J_A=K_A=0 \text{ and } J_B=K_B=1$$

$$A B = 0 \text{ 1, } x = 0 \rightarrow J_A = K_A = 0 \text{ and } J_B = K_B = 1$$

$$J_A = x \quad K_A = xB'$$

$$J_B = K_B = x + A'$$

$$z = A + B$$


Table 6.8b State table with A^* entered.

A B	A* B*		z
	x = 0	x = 1	
0 0	0	1	0
0 1	0	1	1
1 0	1	0	1
1 1	1	1	1

Table 6.8c Completed state table.

A B	A* B*		z
	x = 0	x = 1	
0 0	0 1	1 1	0
0 1	0 0	1 0	1
1 0	1 0	0 1	1
1 1	1 1	1 0	1

Figure 6.25 State diagram for Table 6.8.

 

Timing trace 6.3 Trace for Table 6.8.

x	0	1	0	1	1	0	
A	0	0	1	1	1	0	0
B	0	0	1	1	0	1	0
z	0	1	0	1	1	1	0

Check the timing diagram in Fig. 6.24

Figure 6.24 Timing diagram for Table 6.8.


 


Figure 6.25 State diagram for Table 6.8.

 

An Example: A Mealy machine

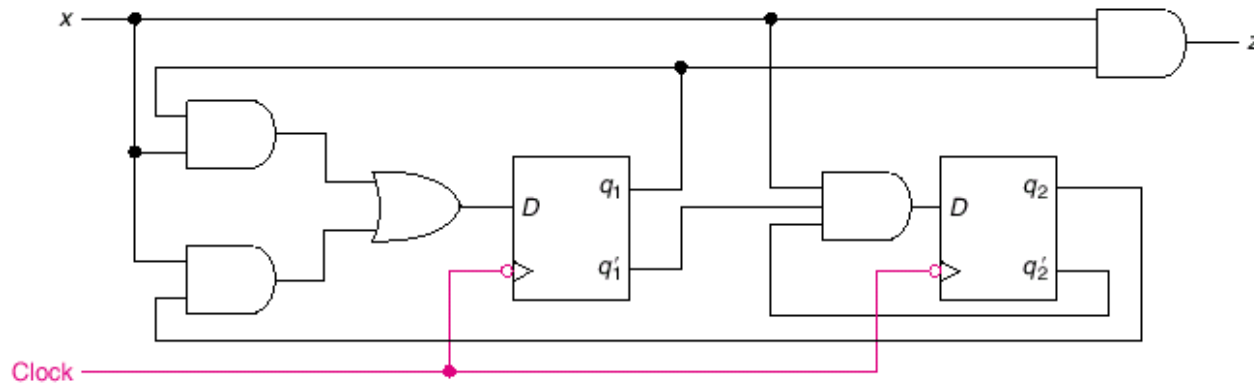


Figure 6.26

1. Logic equation

$$D_1 = xq_1 + xq_2$$

$$D_2 = xq_1'q_2'$$

$$z = xq_1$$

$$q_1^* = xq_1 + xq_2$$

$$q_2^* = xq_1'q_2'$$

2. State table

q	q*		z	
	x = 0	x = 1	x = 0	x = 1
0 0	0 0	0 1	0	0
0 1	0 0	1 0	0	0
1 0	0 0	1 0	0	1
1 1	0 0	1 0	0	1

Table 6.9

3. State diagram

 


Figure 6.27


4. Read the state diagram

- CE 6의 해. (3개의 연속된 1을 체크)
- state "11" is unreachable
- 3 states problem
- 초기화를 하지 않아도 처음 0 이 입력된 후 정상 동작

5. Simulation results : timing diagram

Glitch in the output <-- Mealy machine

Figure 6.28

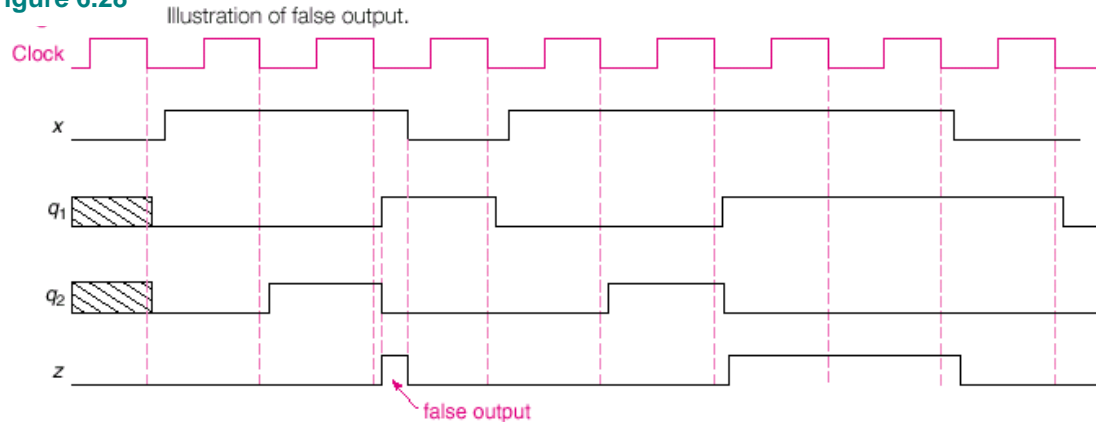

HWork example 6.1, 6.2