

## Design LD Driver


### Design LD Driver with

- 1 12-bits binary counter I\_Out (Predefined value of I\_out is 2000)
- 1 structured module Counter\_1E6
- 3 External input(main input) SW\_ON, LD\_ON, 12-bits I\_set
- 2 12 bits Flip-Flop I\_set\_reg, I\_incr
- 1 Flip-Flop LD\_ON\_reg
- 1 Master Clock 100MHZ (period = 10ns)

### States


- initial state :  $S_0$
- increase I\_out :  $S_1$
- decrease I\_out :  $S_2$
- keep I\_out :  $S_3$
- set high value from  $S_3$  :  $S_4$
- set low value from  $S_3$  :  $S_5$

### Module Structure

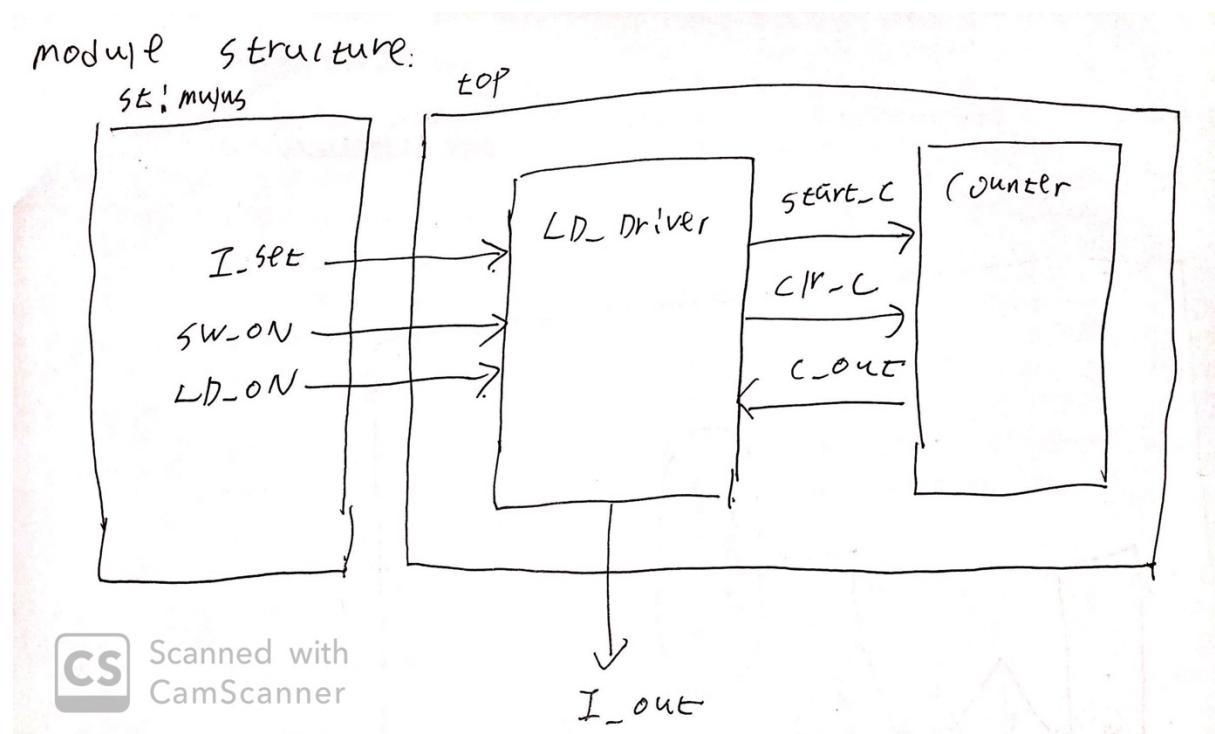
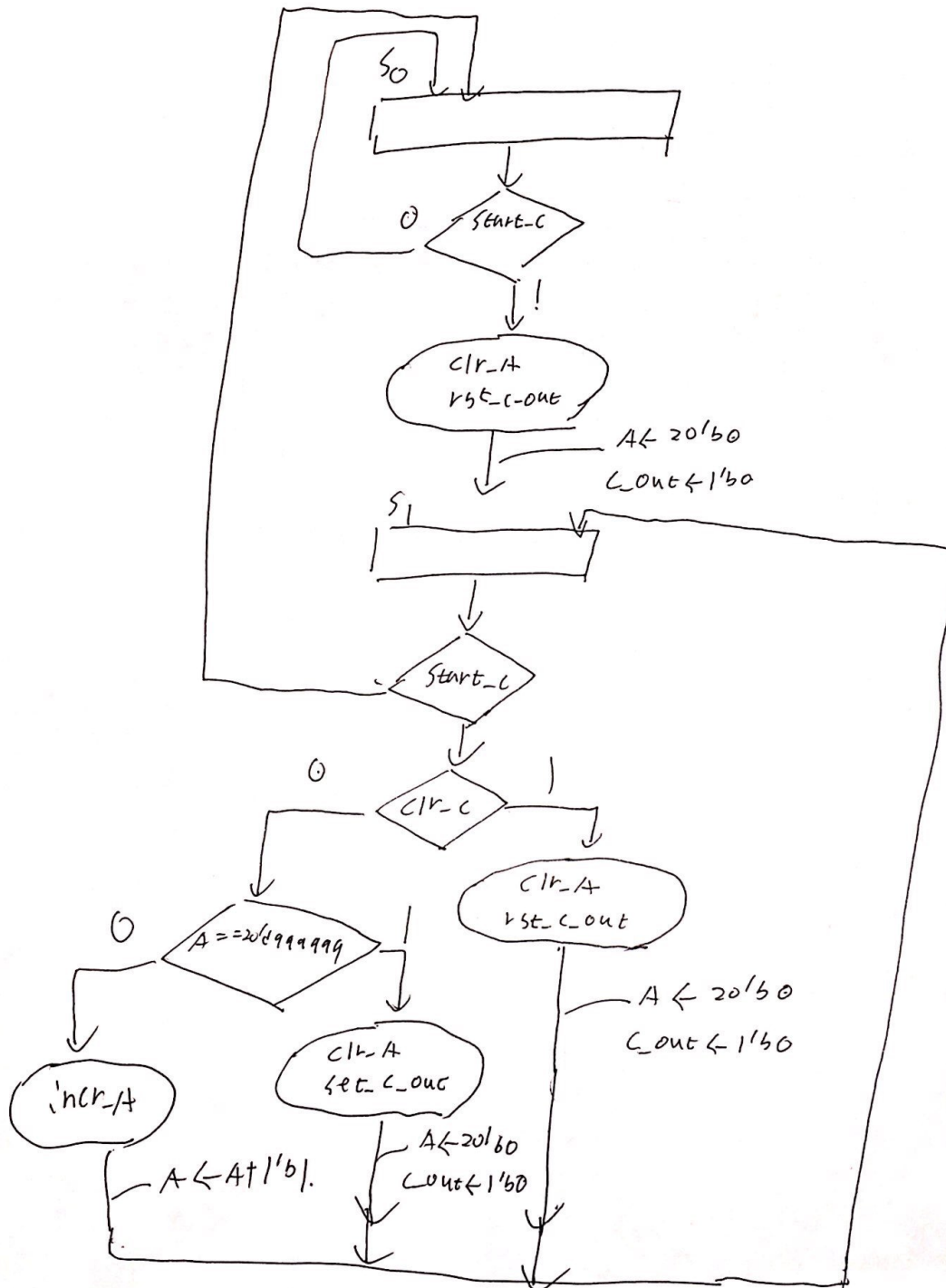
# ASMD Chart of Counter\_1E6

Counter ASMD Chart  $S_0 = 2'b00$   
 $S_1 = 2'b11$




# ASMD Chart of LD\_Driver


ASMD chart  
LD-Driver

S0 = 3'b0001	S3 = 3'b011
S1 = 3'b001	S4 = 3'b100
S2 = 3'b010	S5 = 3'b101


All state

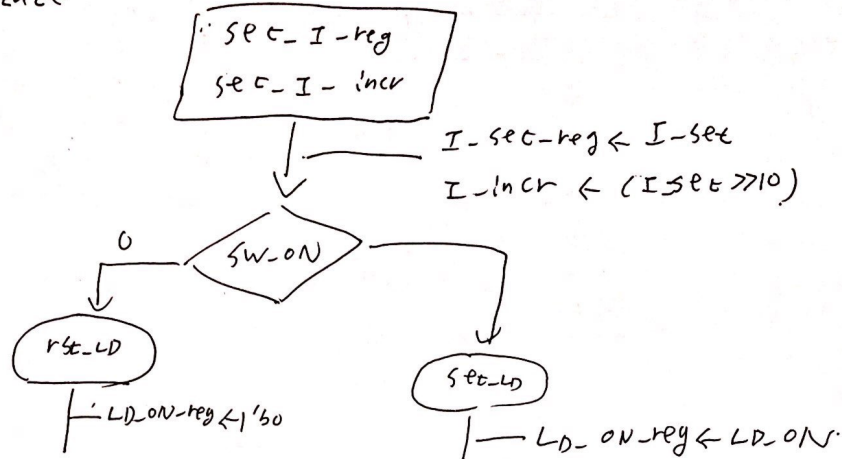


S0 : initial state.

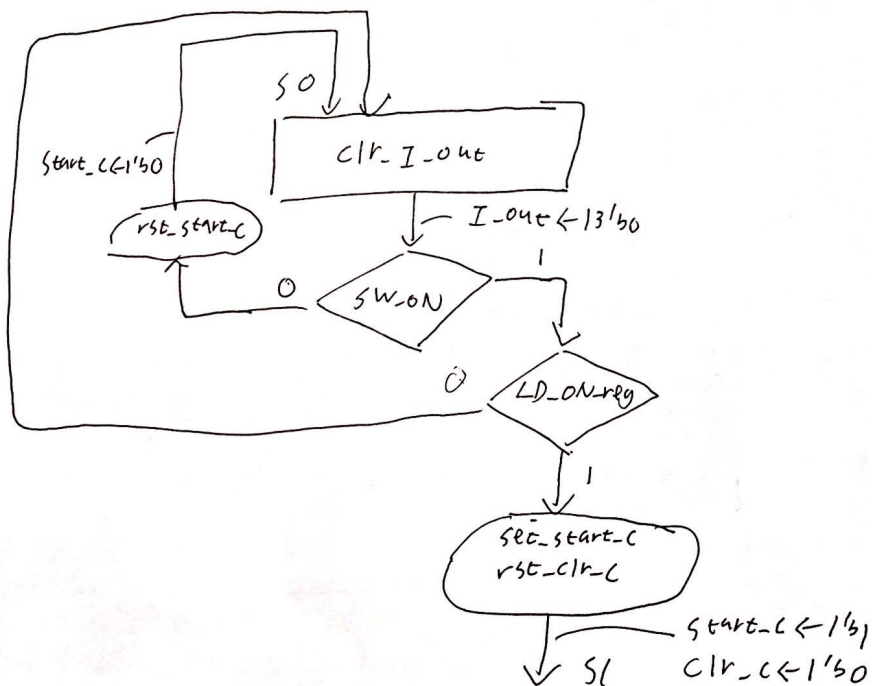

S1 Increase I\_out

 


S2 Decrease I\_out

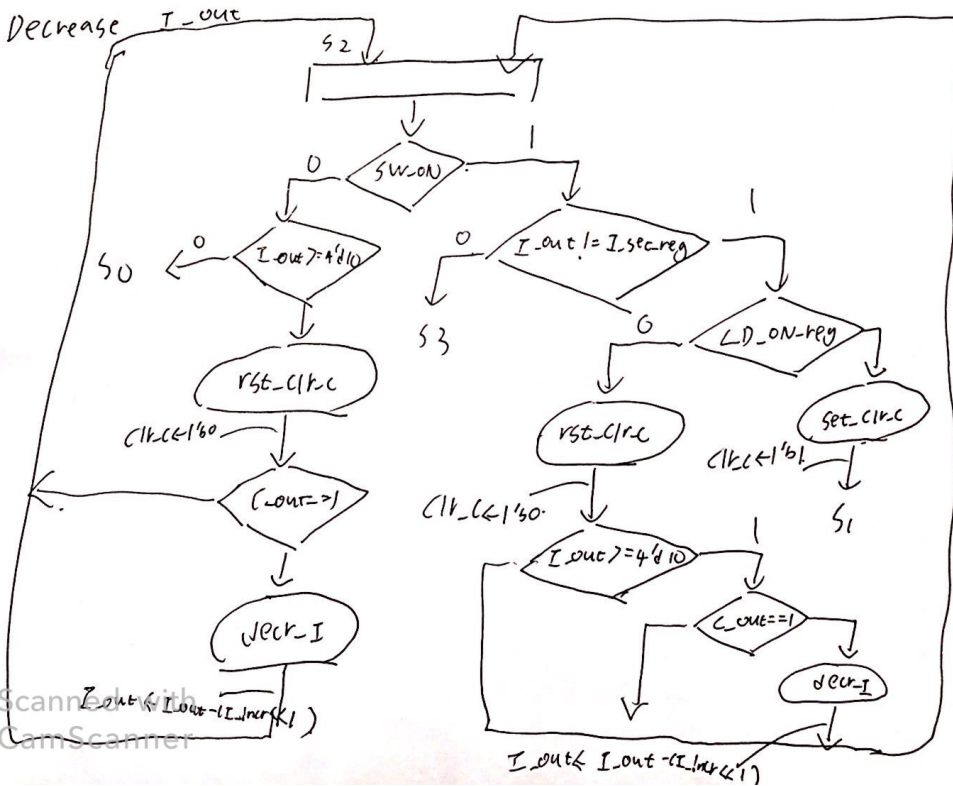


Scanned with  
CamScanner


S3 keep I-out

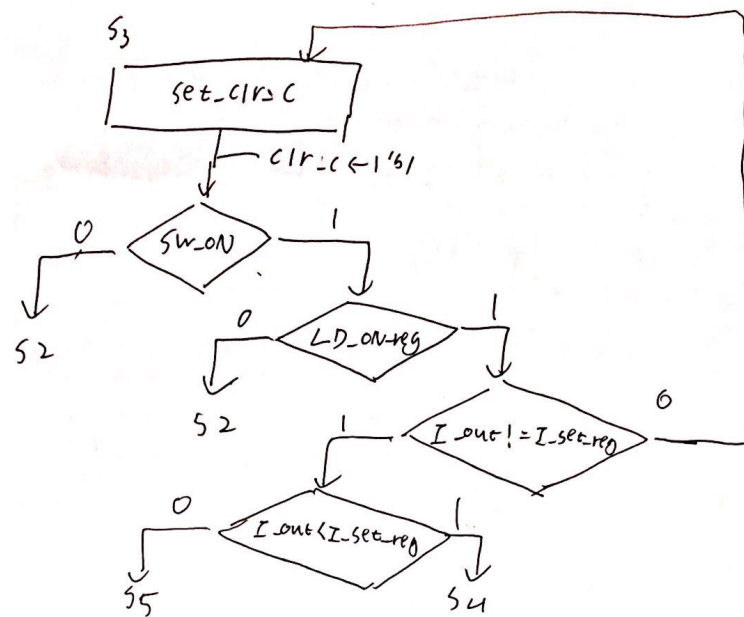

S4 set high value from S3

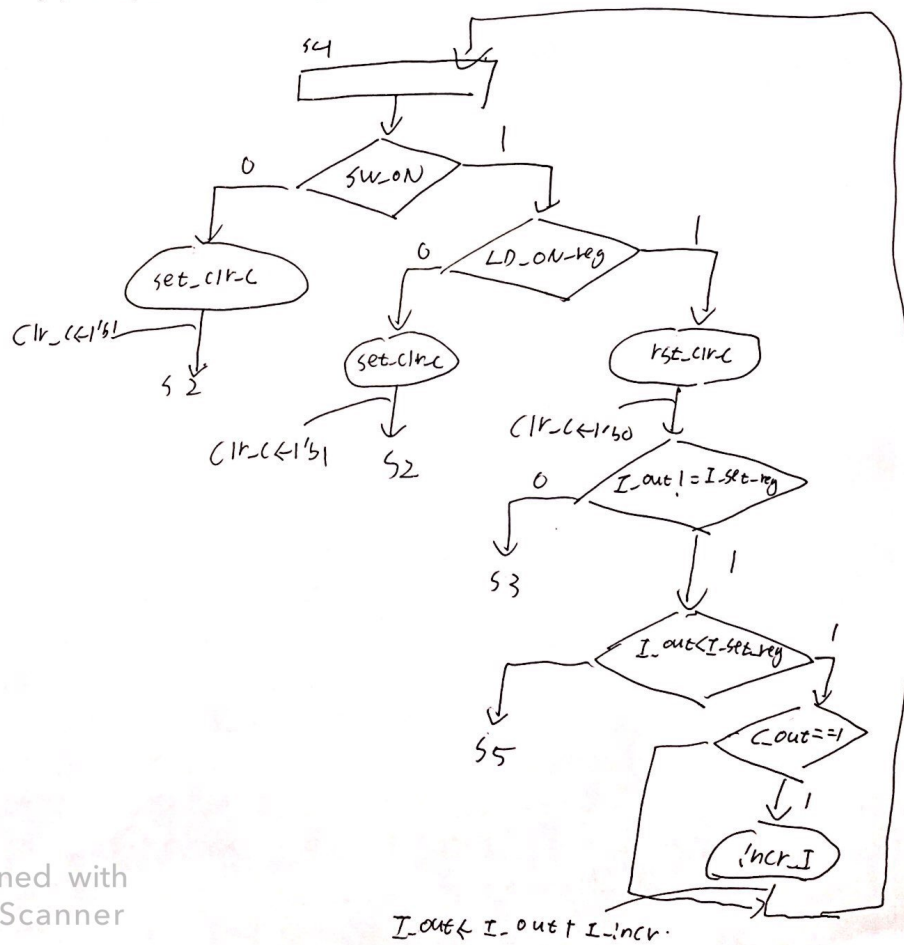

S5 set low value from S3

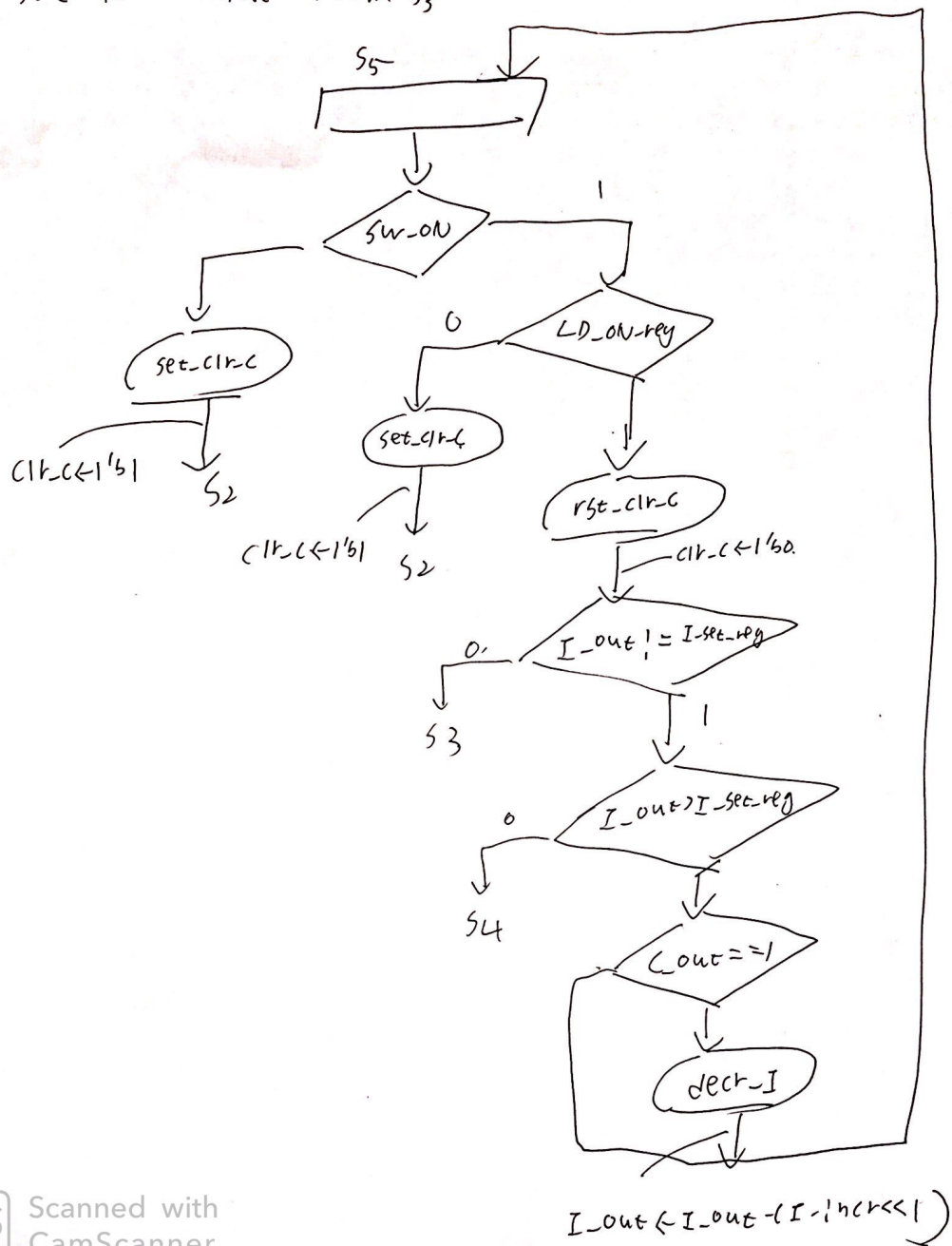

## Verilog

### **top.v**

```
module top(  
    output [12:0] I_out,  
    input [12:0] I_set,  
    input SW_ON, LD_ON,  
    input CLK, Clrn  
);  
    wire Start_C, Clr_C, C_out;  
  
    Counter_1E6_ASM_v_jin C1 (  
        .C_out(C_out),  
        .Start_C(Start_C),  
        .Clr_C(Clr_C),  
        .CLK(CLK),  
        .Clrn(Clrn));  
  
    LD_Driver_ASM_v_jin LD1 (  
        .I_out(I_out),  
        .Start_C(Start_C),  
        .Clr_C(Clr_C),  
        .I_set(I_set),  
        .SW_ON(SW_ON),  
        .LD_ON(LD_ON),  
        .C_out(C_out),  
        .CLK(CLK),  
        .Clrn(Clrn));  
endmodule
```

### **Counter\_1E6\_ASMD\_v\_jin.v**

```
module Counter_1E6_ASMD_v_jin(  
    output reg C_out,  
    input CLK, Clrn  
);
```

```

reg [19:0] A; //Counter_1E6
reg [1:0] pstate, nstate; // state
reg clr_A, incr_A, rst_C_out, set_C_out;

//S0 : initial state, S1 : count
parameter S0 = 2'b00, S1=2'b11;

// state transition for control logic
always @(posedge CLK, negedge Clrn) begin
    if(~Clrn) pstate <= S0;
    else pstate <= nstate; //clocked operation
end

// code next state logic
always@(pstate, A) begin
    case(pstate)
        S0:
            nstate <= S1;
        S1:
            if(A==20'd999999) nstate <= S0;
            else nstate <= S1;
    endcase
end

//code output logic
always@(pstate, A) begin
    clr_A <= 1'b0;
    incr_A <= 1'b0;
    rst_C_out <= 1'b0;
    set_C_out <= 1'b0;
    case(pstate)
        S0:
            clr_A <= 1'b1;
            rst_C_out <= 1'b1;
        S1:
            if(A==20'd999999) begin

```



```

        clr_A <= 1'b1;
        set_C_out <= 1'b1;
    end
    else begin
        incr_A <= 1'b1;
        rst_C_out <= 1'b1;
    end
endcase
end

//Register operation
always @ (posedge CLK, negedge Clrn ) begin
    if(~Clrn) begin
        A <= 20'b0;
        clr_A <= 1'b0;
        incr_A <= 1'b0;
        rst_C_out <= 1'b0;
        set_C_out <= 1'b0;
    end
    else begin
        if(clr_A) A <= 20'b0;
        if(incr_A) A <= A+ 1'b1;
        if(rst_C_out) C_out <= 1'b0;
        if(set_C_out) C_out <= 1'b1;
    end
end
endmodule

```

### LD\_Driver\_ASMD\_v\_jin.v

```

module LD_Driver_ASMD_v_jin(
    output reg [12:0] I_out,
    output reg Start_C,
    output reg Clr_C,
    input [12:0] I_set,
    input SW_ON, LD_ON, C_out,
    input CLK, Clrn

```

```

);
reg LD_ON_reg; // store LD_ON
reg [12:0] I_set_reg; //store i_set value
reg [12:0] I_incr; // setting incremental
reg [2:0] pstate, nstate;
reg set_I_reg, set_I_incr, rst_LD, set_LD, clr_I_out, rst_Start_C, set_Start_C,
rst_Clr_C, set_Clr_C, incr_I, decr_I;
//Encode the states
parameter S0=3'b000, S1=3'b001, S2=3'b010, S3=3'b011, S4=3'b100,
S5=3'b101;

//state transition
always @(posedge CLK, negedge Clrn) begin
    if(~Clrn) pstate <= S0;
    else pstate <= nstate; //clocked operation
end

// code next state logic
always @(SW_ON, LD_ON_reg, pstate, I_out, I_set_reg) begin
    case(pstate)
        S0:
            begin
                if(SW_ON & LD_ON_reg) nstate <= S1;
                else nstate <= S0;
            end

        S1:
            begin
                if(SW_ON & LD_ON_reg) begin
                    if(I_out >= I_set_reg) nstate <= S3;
                    else nstate <= S1;
                end
                else nstate <= S2;
            end

        S2:
            begin

```

```

        if(SW_ON) begin
            if(LD_ON_reg) nstate <= S1;
            else nstate <= S2;
        end
    else
        if(I_out <= 4'b1010) nstate <= S0;
        else nstate <= S2;
    end

default:
begin
    if(SW_ON & LD_ON_reg) begin
        if (I_out != I_set_reg) begin
            if(I_out < I_set_reg) nstate <= S4; //i_set incr
            else nstate <= S5;
        end
        else nstate <= S3;
    end
    else nstate <= S2;
end
endcase
end

always @(SW_ON, LD_ON_reg, pstate, I_out, I_set_reg) begin

    // default assignment
    rst_LD <= 1'b0;
    set_LD <= 1'b0;
    clr_I_out <= 1'b0;
    rst_Start_C <= 1'b0;
    set_Start_C <= 1'b0;
    rst_Clr_C <= 1'b0;
    set_Clr_C <= 1'b0;
    incr_I <= 1'b0;
    decr_I <= 1'b0;

    // if SW_ON == 0, set LD_ON_reg 1'b0

```

```
if (SW_ON) set_LD <= 1'b1;
else rst_LD <= 1'b1;
set_I_reg <= 1'b1; // store i_set
set_I_incr <= 1'b1; // divide by 1024(approx 1000)
```

```
case (pstate)
```

```
  S0:
```

```
  begin
```

```
    clr_I_out <= 1'b1;
```

```
    if(SW_ON) begin
```

```
      set_Start_C <= 1'b1;
```

```
      rst_Clr_C <= 1'b1;
```

```
    end
```

```
    else rst_Start_C <= 1'b1;
```

```
  end
```

```
  S1:
```

```
  begin
```

```
    if(SW_ON) begin
```

```
      if(LD_ON_reg) begin
```

```
        rst_Clr_C <= 1'b1;
```

```
        if(I_out < I_set_reg) begin
```

```
          if(C_out == 1'b1) begin
```

```
            incr_I <= 1'b1;
```

```
          end
```

```
        end
```

```
      end
```

```
      else Clr_C <= 1'b1;
```

```
    end
```

```
    else Clr_C <= 1'b1;
```

```
  end
```

```
  S2:
```

```
  begin
```

```
    if(SW_ON) begin
```

```
      if(!LD_ON_reg) begin
```

```
        rst_Clr_C <= 1'b1;
```

```

        if(I_out >= 4'b1010) begin
            if(C_out == 1'b1) begin
                //multiple by 2
                decr_I <= 1'b1;
            end
        end
    end
end
else Clr_C <= 1'b1;
end
else begin
    if(I_out >= 4'b1010) begin
        rst_Clr_C <= 1'b1;
        if(C_out == 1'b1) begin
            decr_I <= 1'b1;
        end
    end
    else Clr_C <= 1'b1;
end
end
end

```

```

S3:
    set_Clr_C <= 1'b1;

```

```

S4:
begin
    if(SW_ON) begin
        if(LD_ON_reg) begin
            rst_Clr_C <= 1'b1;
            if(I_out < I_set_reg) begin
                if(C_out == 1'b1) begin
                    incr_I <= 1'b1;
                end
            end
        end
    end
    else Clr_C <= 1'b1;
end
else Clr_C <= 1'b1;

```

```

end

S5:
begin
    if(SW_ON) begin
        if(LD_ON_reg) begin
            rst_Clr_C <= 1'b1;
            if(I_out > I_set_reg) begin
                if(C_out == 1'b1) begin
                    decr_I <= 1'b1;
                end
            end
        end
    end
    else Clr_C <= 1'b1;
end
else Clr_C <= 1'b1;
end
endcase
end

//Register Transfer operation
always @ ( posedge CLK, negedge Clrn ) begin
    if(~Clrn) begin
        L_out <= 13'b0;
        LD_ON_reg <= 1'b0;
        L_set_reg <= 13'b0;
        L_incr <= 13'b0;
    end
    else begin
        if(set_I_reg) L_set_reg <= I_set; //store i value
        if(set_I_incr) L_incr <= (I_set >> 10); // make incr
        if(rst_LD) LD_ON_reg <= 1'b0;
        if(set_LD) LD_ON_reg <= LD_ON;
        if(clr_I_out) L_out <= 13'b0;
        if(rst_Start_C) Start_C <= 1'b0;
        if(set_Start_C) Start_C <= 1'b1;
        if(rst_Clr_C) Clr_C <= 1'b0;
    end
end

```

```

        if(set_Clr_C) Clr_C <= 1'b1;
        if(incr_I) I_out <= I_out + I_incr;
        if(decr_I) I_out <= I_out - (I_incr << 1);
    end
end
endmodule

```

## sti.v

```

`timescale 1ns/1ns
module sti;

    reg CLK, Clrn;
    reg [12:0] I_set;
    wire [12:0] I_out;
    reg SW_ON, LD_ON;

    //set end time
    initial begin
        #40E6 $finish;
    end

    initial
    begin
        CLK <= 1'b0;
        Clrn <= 1'b0;
        SW_ON <= 1'b1;
        LD_ON <= 1'b1;
        I_set <= 13'd1024;
        #20 Clrn <= 1'b1; // reset two clock edge
        #5E6 I_set <= 13'd2048;
        #2E6 I_set <= 13'd1024;
        #4E6 I_set <= 13'd2048;
        #8E6 I_set <= 13'd1024;
        #6E6 LD_ON <= 1'b0; //start decreasing
        #3E6 I_set <= 13'd2048;
        #2E6 I_set <= 13'd1024;
    end
endmodule

```

```

        #2E6 LD_ON <= 1'b1; //again start increasing
        #2E6 SW_ON <= 1'b0; //turn off the switch
        #1E6 SW_ON <= 1'b1; //again switch on
    end

    always #5 CLK <= ~CLK; //clock generator

    top t1 (
        .I_out(I_out),
        .I_set(I_set),
        .SW_ON(SW_ON),
        .LD_ON(LD_ON),
        .CLK(CLK),
        .Clrn(Clrn));


    always @(I_out) begin
        $monitor("I_out = %d, time = %0d", I_out, $time);
    end
endmodule

```




## RTL Simulation

### 1) Increasing I\_out

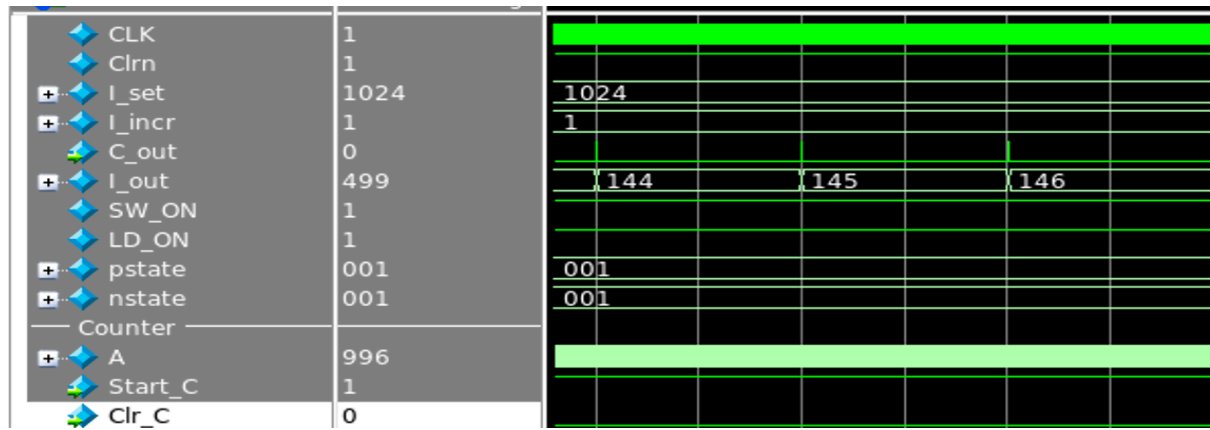

SW\_ON = 1  
LD\_ON = 1  
LD\_ON\_reg = 1  
I\_set = 1024  
I\_incr = 1  
State : S1 (001)
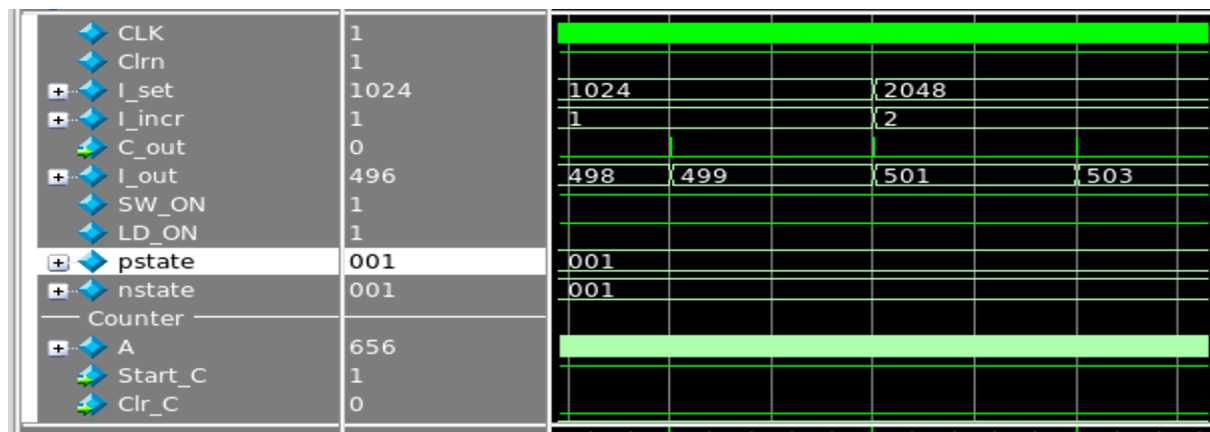
### 2) change I\_set during increasing I\_out



SW\_ON = 1  
LD\_ON = 1  
LD\_ON\_reg = 1  
I\_set = 2048  
I\_incr = 2  
State : S1 (001)

3) change again  $I_{set}$  during increasing  $I_{out}$

CLK	1					
Clrn	1					
$I_{set}$	2048	2048		1024		
$I_{incr}$	2	2		1		
$C_{out}$	0					
$I_{out}$	887	897	899	900	901	
SW_ON	1					
LD_ON	1					
pstate	001	001				
nstate	001	001				
Counter						
A	142					
Start_C	1					
Clr_C	0					


SW\_ON = 1  
LD\_ON = 1  
LD\_ON\_reg = 1  
 $I_{set}$  = 1024  
 $I_{incr}$  = 1  
State : S1 (001)

4) reach  $I_{set}$  value

CLK	0					
Clrn	1					
$I_{set}$	1024	1024				
$I_{incr}$	1	1				
$C_{out}$	0					
$I_{out}$	1024	1022	1023	1024		
SW_ON	1					
LD_ON	1					
pstate	011	001		011		
nstate	011	001		011		
Counter						
A	0			0		
Start_C	1					
Clr_C	1					


SW\_ON = 1  
LD\_ON = 1  
LD\_ON\_reg = 1  
 $I_{set}$  = 1024  
 $I_{incr}$  = 1  
State : S3 (011)

 5) change High value of I\_set when keep I\_out




SW\_ON = 1  
 LD\_ON = 1  
 LD\_ON\_reg = 1  
 I\_set = 2048  
 I\_incr = 2  
 State : S4 (100)

6) reach High value of I\_set

 

SW\_ON = 1  
 LD\_ON = 1  
 LD\_ON\_reg = 1  
 I\_set = 2048  
 I\_incr = 2  
 State : S3 (011)

 7) change low value of I\_set when keep I\_out



SW\_ON = 1

LD\_ON = 1


LD\_ON\_reg = 1

I\_set = 1024

I\_incr = 1 (I\_decr : 2)

State : S5 (101)

8) Decreasing I\_out when LD\_ON is 0

 

SW\_ON = 1

LD\_ON = 0


LD\_ON\_reg = 0

I\_set = 1024

I\_incr = 1 (I\_decr : 2)

State : S2 (010)

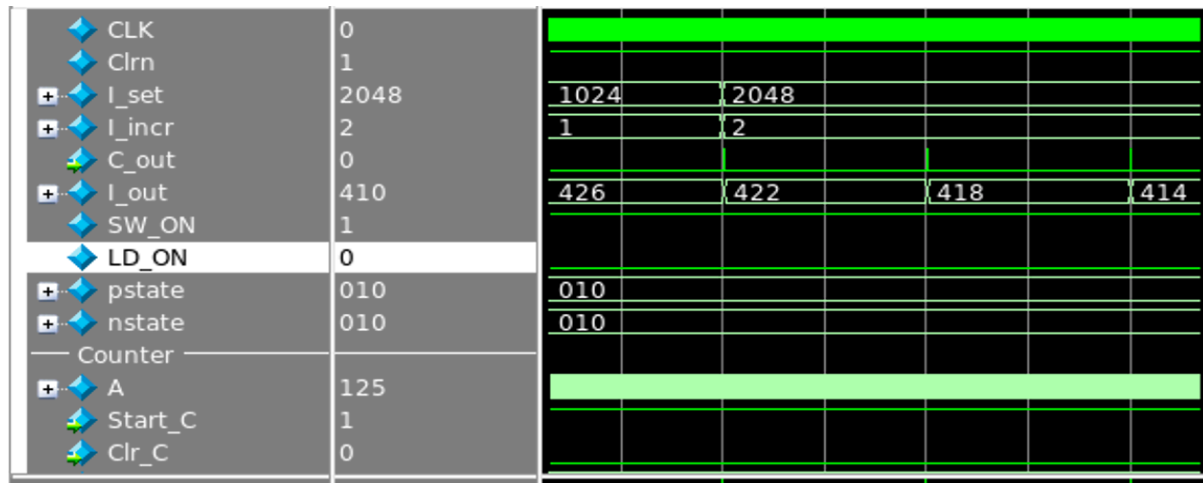9) change I\_set during decreasing I\_out



SW\_ON = 1

LD\_ON = 0


LD\_ON\_reg = 0

I\_set = 2048

I\_incr = 2 (I\_decr : 4)

State : S2 (010)

 10) keep I\_out below 10 and stay in switch on



SW\_ON = 1

LD\_ON = 0


LD\_ON\_reg = 0

I\_set = 2048

I\_incr = 2 (I\_decr : 4)

State : S2 (010)

11) change LD\_ON to 1

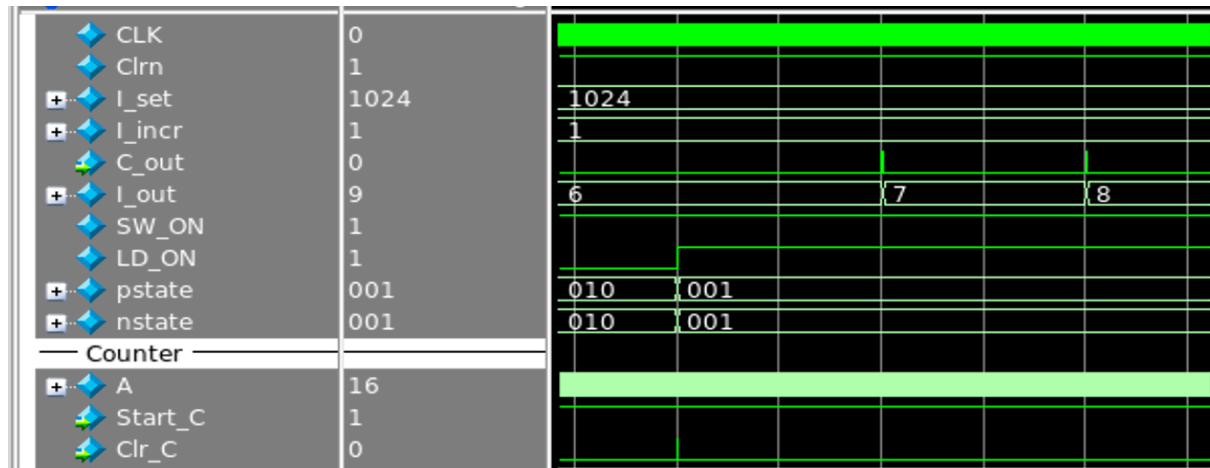

SW\_ON = 1

LD\_ON = 1


LD\_ON\_reg = 1

I\_set = 1024

I\_incr = 1 (I\_decr : 2)

State : S1 (001)

12) Switch off

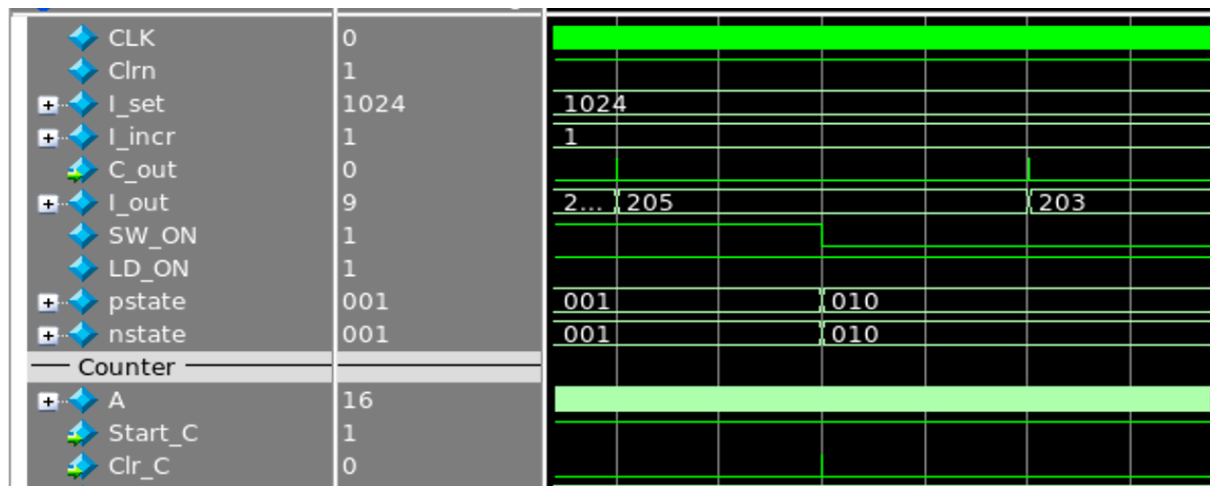

SW\_ON = 0

LD\_ON = 1


LD\_ON\_reg = 0

I\_set = 1024

I\_incr = 1 (I\_decr : 2)

State : S2 (010)

 13) When I\_out reaches below 10, initialize I\_out to 0 and go to initial state



SW\_ON = 0

LD\_ON = 1


LD\_ON\_reg = 0

I\_set = 1024

I\_incr = 1 (I\_decr : 2)

State : S0 (000)

14) Switch on again

 

SW\_ON = 1

LD\_ON = 1

LD\_ON\_reg = 1

I\_set = 1024

I\_incr = 1

State : S1 (001)

자기 평가:

수업시간에 배운 ASM, ASMD 차트로 실제 생활에 이용할 법한 것을 제작 및 설계를 해보니 코딩 실력 뿐만 아니라 어떻게 설계 해야하는지에 대해 많이 배운 것 같다. 이전에는 디지털 시계를 만드는 간단한 것만 설계할 수 있었는데 지금은 원하는 디자인 어떠한 것을 요구해도 수업에 배운 Design Process 를 따라가면 무엇이든지 만들 수 있을 것 같다는 자신감이 든다. 또한 쿼터스라는 툴을 직접 이용해보고 여러가지 결과를 확인하며 코드를 디버깅하는 능력도 향상된 것 같아서 매우 좋은 수업이었고, 수업을 떠나 이후 베릴로그 코딩 실력이 매우 높아진 것 같다.