

Case 1)

pstate = 0 (blocking assignment)

always (S, A, pstate) no else block

Flow Summary	
Flow Status	Successful - Fri Nov 15 03:16:00 2015
Quartus Prime Version	15.1.0 Build 185 10/21/2015 SJ Lit
Revision Name	RTL_Ex_8_2_v_jin
Top-level Entity Name	RTL_Ex_8_2_v_jin
Family	Cyclone IV E
Device	EP4CE10E22C6
Timing Models	Final
Total logic elements	18 / 10,320 (< 1 %)
Total combinational functions	14 / 10,320 (< 1 %)
Dedicated logic registers	9 / 10,320 (< 1 %)
Total registers	9
Total pins	9 / 92 (10 %)
Total virtual pins	0
Total memory bits	0 / 423,936 (0 %)
Embedded Multiplier 9-bit elements	0 / 46 (0 %)
Total PLLs	0 / 2 (0 %)

Analysis & Synthesis Resource Usage Summary		
	Resource	
1	Estimated Total logic elements	14
2		
3	Total combinational functions	14
4	▼ Logic element usage by number of LUT inputs	
1	-- 4 input functions	4
2	-- 3 input functions	6
3	-- <=2 input functions	4
5		
6	▼ Logic elements by mode	
1	-- normal mode	14
2	-- arithmetic mode	0
7		
8	▼ Total registers	9
1	-- Dedicated logic registers	9
2	-- I/O registers	0
9		
10	I/O pins	9

- 17049 1 registers lost all their fanouts during netlist optimizations.
- 16010 Generating hard_block partition "hard_block:auto_generated_inst"
- 21057 Implemented 22 device resources after synthesis - the final resource count might be different
- Quartus Prime Analysis & Synthesis was successful. 0 errors, 15 warnings

Estimated Total logic elements : 14

Total Combinational functions : 14

Total Registers : 9

Case 2)

pstate <= 0 (blocking assignment)

always (S, A, pstate) no else block

```

1 module RTL_Ex_8_2_v_jin(
2     output reg E, F,
3     output reg[3:0] A,
4     input S, CLK, Clrn
5 );
6 //specify system registers
7 reg [1:0] pstate, nstate; //control register
8 //Encode the states
9 parameter T0 = 2'b00, T1 = 2'b01, T2 = 2'b10;
10 //state transition for control
11 always @(posedge CLK, negedge Clrn) begin
12     if(~Clrn) pstate <= T0; //initial state
13     else pstate <= nstate; //colcked operations
14 end
15
16 //decision box -> decide next state
17 always @(S, A, pstate) begin
18     case(pstate)
19     T0:
20     begin
21         if(S) nstate = T1;
22     end
23     T1:
24     begin
25         if(A[2]&A[3]) nstate = T2;
26     end
27     T2:
28     begin
29         nstate = T0;
30     end
31     endcase
32 end
33

```

Flow Summary	
Flow Status	Successful - Fri Nov 15 03:16:00 2
Quartus Prime Version	15.1.0 Build 185 10/21/2015 SJ Lit
Revision Name	RTL_Ex_8_2_v_jin
Top-level Entity Name	RTL_Ex_8_2_v_jin
Family	Cyclone IV E
Device	EP4CE10E22C6
Timing Models	Final
Total logic elements	18 / 10,320 (< 1 %)
Total combinational functions	14 / 10,320 (< 1 %)
Dedicated logic registers	9 / 10,320 (< 1 %)
Total registers	9
Total pins	9 / 92 (10 %)
Total virtual pins	0
Total memory bits	0 / 423,936 (0 %)
Embedded Multiplier 9-bit elements	0 / 46 (0 %)
Total PLLs	0 / 2 (0 %)

Analysis & Synthesis Resource Usage Summary		
	Resource	
1	Estimated Total logic elements	14
2		
3	Total combinational functions	14
4	▼ Logic element usage by number of LUT inputs	
1	-- 4 input functions	4
2	-- 3 input functions	6
3	-- <=2 input functions	4
5		
6	▼ Logic elements by mode	
1	-- normal mode	14
2	-- arithmetic mode	0
7		
8	▼ Total registers	9
1	-- Dedicated logic registers	9
2	-- I/O registers	0
9		
10	I/O pins	9

Estimated Total logic elements : 14

Total Combinational functions : 14

Total Registers : 9

Case 1) 과 차이 없음

Case 3)

always (S, A, pstate) have all else block

```

1 module RTL_Ex_8_2_v_jin(
2     output reg E, F,
3     output reg[3:0] A,
4     input S, CLK, Clnr
5 );
6 //specify system registers
7 reg [1:0] pstate, nstate; //control register
8 //Encode the states
9 parameter T0 = 2'b00, T1 = 2'b01, T2 = 2'b10;
10 //state transition for control
11 always @(posedge CLK, negedge Clnr) begin
12     if(!Clnr) pstate <= T0; //initial state
13     else pstate <= nstate; //colcked operations
14 end
15
16 //decision box -> decide next state
17 always @(S, A, pstate) begin
18     case(pstate)
19         T0:
20             begin
21                 if(S) nstate = T1;
22                 else nstate = T0;
23             end
24         T1:
25             begin
26                 if(A[2]&A[3]) nstate = T2;
27                 else nstate = T1;
28             end
29         T2:
30             begin
31                 nstate = T0;
32             end
33     endcase
34 end

```

Flow Summary	
Flow Status	Successful - Thu Nov 14 22:38:10
Quartus Prime Version	15.1.0 Build 185 10/21/2015 SJ Lit
Revision Name	RTL_Ex_8_2_v_jin
Top-level Entity Name	RTL_Ex_8_2_v_jin
Family	Cyclone IV E
Device	EP4CE10E22C6
Timing Models	Final
Total logic elements	12 / 10,320 (< 1 %)
Total combinational functions	11 / 10,320 (< 1 %)
Dedicated logic registers	9 / 10,320 (< 1 %)
Total registers	9
Total pins	9 / 92 (10 %)
Total virtual pins	0
Total memory bits	0 / 423,936 (0 %)
Embedded Multiplier 9-bit elements	0 / 46 (0 %)
Total PLLs	0 / 2 (0 %)

Analysis & Synthesis Resource Usage Summary		
	Resource	
1	Estimated Total logic elements	11
2		
3	Total combinational functions	11
4	▼ Logic element usage by number of LUT inputs	
1	-- 4 input functions	4
2	-- 3 input functions	4
3	-- <=2 input functions	3
5		
6	▼ Logic elements by mode	
1	-- normal mode	11
2	-- arithmetic mode	0
7		
8	▼ Total registers	9
1	-- Dedicated logic registers	9
2	-- I/O registers	0
9		
10	I/O pins	9

Estimated Total logic elements : 11 (3 개 감소)

Total Combinational functions : 11

Total Registers : 9

Case 4)

always (S, A, pstate) all non-block assignment

<pre> 1 module RTL_Ex_8_2_v_jin(2 output reg E, F, 3 output reg[3:0] A, 4 input S, CLK, Clrn 5); 6 //specify system registers 7 reg [1:0] pstate, nstate; //control register 8 //Encode the states 9 parameter T0 = 2'b00, T1 = 2'b01, T2 = 2'b10; 10 //state transition for control 11 always @(posedge CLK, negedge Clrn) begin 12 if(~Clrn) pstate <= T0; //initial state 13 else pstate <= nstate; //colcked operations 14 end 15 16 //decision box -> decide next state 17 always @(S, A, pstate) begin 18 case(pstate) 19 T0: 20 begin 21 if(S) nstate <= T1; 22 else nstate <= T0; 23 end 24 T1: 25 begin 26 if(A[2]&A[3]) nstate <= T2; 27 else nstate <= T1; 28 end 29 T2: 30 begin 31 nstate <= T0; 32 end 33 endcase 34 end </pre>	<table> <tr> <th colspan="2">Flow Summary</th></tr> <tr> <td>Flow Status</td><td>Successful - Fri Nov 15 03:09:29 2</td></tr> <tr> <td>Quartus Prime Version</td><td>15.1.0 Build 185 10/21/2015 SJ Lite</td></tr> <tr> <td>Revision Name</td><td>RTL_Ex_8_2_v_jin</td></tr> <tr> <td>Top-level Entity Name</td><td>RTL_Ex_8_2_v_jin</td></tr> <tr> <td>Family</td><td>Cyclone IV E</td></tr> <tr> <td>Device</td><td>EP4CE10E22C6</td></tr> <tr> <td>Timing Models</td><td>Final</td></tr> <tr> <td>Total logic elements</td><td>12 / 10,320 (< 1 %)</td></tr> <tr> <td> Total combinational functions</td><td>11 / 10,320 (< 1 %)</td></tr> <tr> <td> Dedicated logic registers</td><td>9 / 10,320 (< 1 %)</td></tr> <tr> <td>Total registers</td><td>9</td></tr> <tr> <td>Total pins</td><td>9 / 92 (10 %)</td></tr> <tr> <td>Total virtual pins</td><td>0</td></tr> <tr> <td>Total memory bits</td><td>0 / 423,936 (0 %)</td></tr> <tr> <td>Embedded Multiplier 9-bit elements</td><td>0 / 46 (0 %)</td></tr> <tr> <td>Total PLLs</td><td>0 / 2 (0 %)</td></tr> </table>	Flow Summary		Flow Status	Successful - Fri Nov 15 03:09:29 2	Quartus Prime Version	15.1.0 Build 185 10/21/2015 SJ Lite	Revision Name	RTL_Ex_8_2_v_jin	Top-level Entity Name	RTL_Ex_8_2_v_jin	Family	Cyclone IV E	Device	EP4CE10E22C6	Timing Models	Final	Total logic elements	12 / 10,320 (< 1 %)	Total combinational functions	11 / 10,320 (< 1 %)	Dedicated logic registers	9 / 10,320 (< 1 %)	Total registers	9	Total pins	9 / 92 (10 %)	Total virtual pins	0	Total memory bits	0 / 423,936 (0 %)	Embedded Multiplier 9-bit elements	0 / 46 (0 %)	Total PLLs	0 / 2 (0 %)
Flow Summary																																			
Flow Status	Successful - Fri Nov 15 03:09:29 2																																		
Quartus Prime Version	15.1.0 Build 185 10/21/2015 SJ Lite																																		
Revision Name	RTL_Ex_8_2_v_jin																																		
Top-level Entity Name	RTL_Ex_8_2_v_jin																																		
Family	Cyclone IV E																																		
Device	EP4CE10E22C6																																		
Timing Models	Final																																		
Total logic elements	12 / 10,320 (< 1 %)																																		
Total combinational functions	11 / 10,320 (< 1 %)																																		
Dedicated logic registers	9 / 10,320 (< 1 %)																																		
Total registers	9																																		
Total pins	9 / 92 (10 %)																																		
Total virtual pins	0																																		
Total memory bits	0 / 423,936 (0 %)																																		
Embedded Multiplier 9-bit elements	0 / 46 (0 %)																																		
Total PLLs	0 / 2 (0 %)																																		

Analysis & Synthesis Resource Usage Summary		
	Resource	
1	Estimated Total logic elements	11
2		
3	Total combinational functions	11
4	▼ Logic element usage by number of LUT inputs	
1	-- 4 input functions	4
2	-- 3 input functions	4
3	-- <=2 input functions	3
5		
6	▼ Logic elements by mode	
1	-- normal mode	11
2	-- arithmetic mode	0
7		
8	▼ Total registers	9
1	-- Dedicated logic registers	9
2	-- I/O registers	0
9		
10	I/O pins	9

Estimated Total logic elements : 11

Total Combinational functions : 11

Total Registers : 9

Case 3) 과 차이 없음

Case 5)

always (S, A, pstate) x'b -> decimal integer

<pre> 36 //register tranfer operations 37 always @(posedge CLK) begin 38 case(pstate) 39 T0: 40 begin 41 if(S) begin 42 A <= 0; 43 F <= 0; 44 end 45 end 46 T1: 47 begin 48 A <= A+1; 49 if(A[3]) begin 50 E <= 1; 51 end 52 else begin 53 E <= 0; 54 end 55 end 56 T2: 57 F <= 1; 58 endcase 59 end 60 endmodule </pre>	<table> <tr> <th colspan="2">Flow Summary</th></tr> <tr> <td>Flow Status</td><td>Successful - Fri Nov 15 03:09:29 2</td></tr> <tr> <td>Quartus Prime Version</td><td>15.1.0 Build 185 10/21/2015 SJ Lit</td></tr> <tr> <td>Revision Name</td><td>RTL_Ex_8_2_v_jin</td></tr> <tr> <td>Top-level Entity Name</td><td>RTL_Ex_8_2_v_jin</td></tr> <tr> <td>Family</td><td>Cyclone IV E</td></tr> <tr> <td>Device</td><td>EP4CE10E22C6</td></tr> <tr> <td>Timing Models</td><td>Final</td></tr> <tr> <td>Total logic elements</td><td>12 / 10,320 (< 1 %)</td></tr> <tr> <td> Total combinational functions</td><td>11 / 10,320 (< 1 %)</td></tr> <tr> <td> Dedicated logic registers</td><td>9 / 10,320 (< 1 %)</td></tr> <tr> <td>Total registers</td><td>9</td></tr> <tr> <td>Total pins</td><td>9 / 92 (10 %)</td></tr> <tr> <td>Total virtual pins</td><td>0</td></tr> <tr> <td>Total memory bits</td><td>0 / 423,936 (0 %)</td></tr> <tr> <td>Embedded Multiplier 9-bit elements</td><td>0 / 46 (0 %)</td></tr> <tr> <td>Total PLLs</td><td>0 / 2 (0 %)</td></tr> </table>	Flow Summary		Flow Status	Successful - Fri Nov 15 03:09:29 2	Quartus Prime Version	15.1.0 Build 185 10/21/2015 SJ Lit	Revision Name	RTL_Ex_8_2_v_jin	Top-level Entity Name	RTL_Ex_8_2_v_jin	Family	Cyclone IV E	Device	EP4CE10E22C6	Timing Models	Final	Total logic elements	12 / 10,320 (< 1 %)	Total combinational functions	11 / 10,320 (< 1 %)	Dedicated logic registers	9 / 10,320 (< 1 %)	Total registers	9	Total pins	9 / 92 (10 %)	Total virtual pins	0	Total memory bits	0 / 423,936 (0 %)	Embedded Multiplier 9-bit elements	0 / 46 (0 %)	Total PLLs	0 / 2 (0 %)
Flow Summary																																			
Flow Status	Successful - Fri Nov 15 03:09:29 2																																		
Quartus Prime Version	15.1.0 Build 185 10/21/2015 SJ Lit																																		
Revision Name	RTL_Ex_8_2_v_jin																																		
Top-level Entity Name	RTL_Ex_8_2_v_jin																																		
Family	Cyclone IV E																																		
Device	EP4CE10E22C6																																		
Timing Models	Final																																		
Total logic elements	12 / 10,320 (< 1 %)																																		
Total combinational functions	11 / 10,320 (< 1 %)																																		
Dedicated logic registers	9 / 10,320 (< 1 %)																																		
Total registers	9																																		
Total pins	9 / 92 (10 %)																																		
Total virtual pins	0																																		
Total memory bits	0 / 423,936 (0 %)																																		
Embedded Multiplier 9-bit elements	0 / 46 (0 %)																																		
Total PLLs	0 / 2 (0 %)																																		

Analysis & Synthesis Resource Usage Summary		
	Resource	
1	Estimated Total logic elements	11
2		
3	Total combinational functions	11
4	▼ Logic element usage by number of LUT inputs	
1	-- 4 input functions	4
2	-- 3 input functions	4
3	-- <=2 input functions	3
5		
6	▼ Logic elements by mode	
1	-- normal mode	11
2	-- arithmetic mode	0
7		
8	▼ Total registers	9
1	-- Dedicated logic registers	9
2	-- I/O registers	0
9		
10	I/O pins	9

Estimated Total logic elements : 11

Total Combinational functions : 11


Total Registers : 9

Case 3) 과 차이 없음

최종 코드 :

```
1 module RTL_Ex_8_2_v_jin(  
2     output reg E, F,  
3     output reg[3:0] A,  
4     input S, CLK, Clrn  
5 );  
6 //specify system registers  
7 reg [1:0] pstate, nstate; //control register  
8 //Encode the states  
9 parameter T0 = 2'b00, T1 = 2'b01, T2 = 2'b10;  
10 //state transition for control  
11 always @(posedge CLK, negedge Clrn) begin  
12     if(~Clrn) pstate <= T0; //initial state  
13     else begin  
14         pstate <= nstate; //clocked operations  
15         case(pstate)  
16             T0:  
17                 begin  
18                     if(S) begin  
19                         A <= 4'b0000;  
20                         F <= 1'b0;  
21                     end  
22                     end  
23             T1:  
24                 begin  
25                     A <= A+4'b0001;  
26                     if(A[2]) begin  
27                         E <= 1'b1;  
28                     end  
29                     else begin  
30                         E <= 1'b0;  
31                     end  
32                     end  
33             T2:  
34                 F <= 1'b1;  
35             endcase  
36         end  
37     end  
38  
39 //decision box -> decide next state  
40 always @(S, A, pstate) begin  
41     case(pstate)  
42         T0:  
43             begin  
44                 if(S) nstate = T1;  
45                 else nstate = T0;  
46             end  
47         T1:  
48             begin  
49                 if(A[2]&A[3]) nstate = T2;  
50                 else nstate = T1;  
51             end  
52         T2:  
53             begin  
54                 nstate = T0;  
55             end  
56         endcase  
57     end  
58 endmodule
```

```
1 module RTL_Ex_8_2_v_jin(  
2     output reg E, F,  
3     output reg[3:0] A,  
4     input S, CLK, Clrn  
5 );  
6 //specify system registers  
7 reg [1:0] pstate, nstate; //control register  
8 //Encode the states  
9 parameter T0 = 2'b00, T1 = 2'b01, T2 = 2'b10;  
10 //state transition for control  
11 always @(posedge CLK, negedge Clrn) begin  
12     if(~Clrn) pstate <= T0; //initial state  
13     else begin  
14         pstate <= nstate; //clocked operations  
15     end  
16 end  
17  
18 //decision box -> decide next state  
19 always @(S, A, pstate) begin  
20     case(pstate)  
21         T0:  
22             begin  
23                 if(S) nstate = T1;  
24                 else nstate = T0;  
25             end  
26         T1:  
27             begin  
28                 if(A[2]&A[3]) nstate = T2;  
29                 else nstate = T1;  
30             end  
31         T2:  
32             begin  
33                 nstate = T0;  
34             end  
35         endcase  
36     end  
37  
38 always @(posedge CLK) begin  
39     case(pstate)  
40         T0:  
41             begin  
42                 if(S) begin  
43                     A <= 4'b0000;  
44                     F <= 1'b0;  
45                 end  
46             end  
47         T1:  
48             begin  
49                 A <= A+4'b0001;  
50                 if(A[2]) begin  
51                     E <= 1'b1;  
52                 end  
53                 else begin  
54                     E <= 1'b0;  
55                 end  
56             end  
57         T2:  
58             F <= 1'b1;  
59         endcase  
60     end
```

 



Register operation 의 $A \leftarrow A + 4'b0001$ 동작에서 carry 가 있을 시 A 의 값이 변화하면서 A register 에 저장된 값이 바뀌며 생기는 delay time 이 존재하는 것을 알았고 이와 마찬가지로 Flip-Flop E, F 도 해당 값이 바뀌면 flip flop 에 의한 delay 가 생기는 것을 알 수 있었다.

코드 상에서 $A \leftarrow A + 1'b1$ 로 바뀌도 같았으며 이는 값이 flip-flop 을 통과하며 생기는 어쩔 수 없는 delay time 이라는 것을 알게 되었다. 그래서 이후 combinational logic 으로 control unit 을 짤 때 combinational 은 기억을 하지 못하므로 나온 결과를 Flip-Flop 에 의도적으로 통과 시켜 Register 와 같은 Delay time 을 주어서 연산을 맞추는 것도 필요 할 것 같다는 생각이 든다.

일반적으로 회로가 돌아가고 첫 edge 에서 두 번째 edge 는 클리어 신호를 주어 회로의 초기값을 지정한다. 하지만 책에 있는 대로 state operation 과 Register operation 을 코드 상에서 분리하면 현재 디자인에서는 문제가 없지만 정확하게 이는 시스템 전체를 초기화 시키는 Clrn 의 의미가 아니다.(단순히 state 만을 초기화) 만약 시스템 전체적으로 초기화를 진행하는 Clrn 이라는 의미의 동작을 행하려면 이런 분리된 코드에서는 Register operation 에서도 negedge Clrn 을 추가해 초기화를 해야 한다. 그렇지 않으면 Clrn 0 일 때에도 Clrn 의 신호를 무시한 채 posedge CLK 일 때 Register operation 은 따로 동작하기에 원하는 시스템 전체적으로 초기화가 진행되지 않을 수 있다. 위의 VWF 결과에서도 확인 할 수 있듯이 Clrn 신호가 들어갔음에도 $A \leftarrow A + 1'b1$ 연산이 수행되는 것을 확인 할 수 있다. 이렇게 되면 resigster operation 이 state operation 과 다른 상태(초기값이 맞춰지지 않은 상태)에서 동작을 수행하기에 원하는 결과가 나오지 않을 수 있다. (Ex. Register 의 조건이 next state 를 결정하는 디자인)

VWF (Timing Sequence 확인)

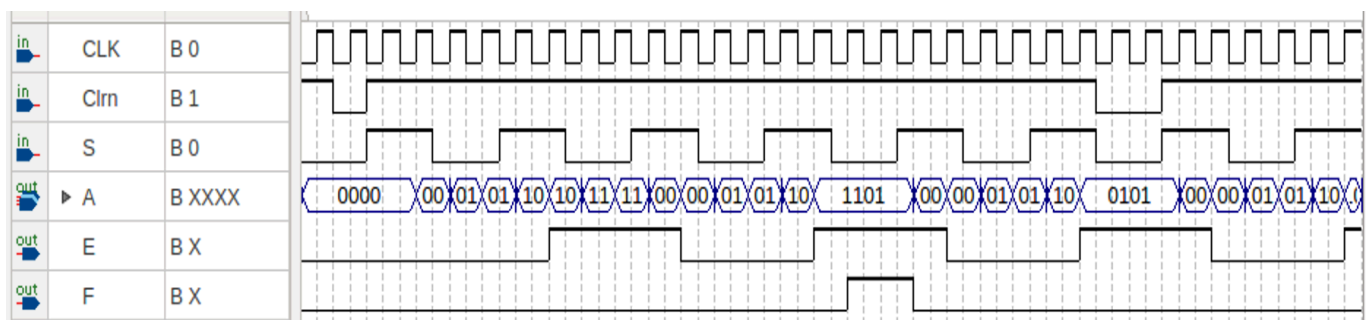

Input		Main input	Counter	FF		Conditions	pstate	nstate	Operations
CLK	Clrn	S	A[3:0]	E	F				
↑	1	0	0000	0	0	$A_3 = 0$ $A_4 = 0$	T_0	T_0	
	↓	0	0000	0	0	$A_3 = 0$ $A_4 = 0$	T_0	T_0	Asynchronous reset
↑	0	0	0000	0	0	$A_3 = 0$ $A_4 = 0$	T_0	T_0	$pstate \leq T_0$
	1	1	0000	0	0	$A_3 = 0$ $A_4 = 0$	T_0	T_1	
↑	1	1	0000	0	0	$A_3 = 0$ $A_4 = 0$	T_1	T_1	$T_0 \rightarrow T_1$ $A \leftarrow 4'b0000$ $F \leftarrow 1'b0$
↑	1	1	0001	0	0	$A_3 = 0$ $A_4 = 0$	T_1	T_1	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b0$
↑	1	0	0010	0	0	$A_3 = 0$ $A_4 = 0$	T_1	T_1	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b0$
↑	1	0	0011	0	0	$A_3 = 0$ $A_4 = 0$	T_1	T_1	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b0$
↑	1	1	0100	0	0	$A_3 = 1$ $A_4 = 0$	T_1	T_1	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b0$
↑	1	1	0101	1	0	$A_3 = 1$ $A_4 = 0$	T_1	T_1	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b1$
↑	1	0	0110	1	0	$A_3 = 1$ $A_4 = 0$	T_1	T_1	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b1$
↑	1	0	0111	1	0	$A_3 = 1$ $A_4 = 0$	T_1	T_1	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b1$
↑	1	1	1000	1	0	$A_3 = 0$ $A_4 = 1$	T_1	T_1	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b1$
↑	1	1	1001	0	0	$A_3 = 0$ $A_4 = 1$	T_1	T_1	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b0$
↑	1	0	1010	0	0	$A_3 = 0$ $A_4 = 1$	T_1	T_1	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b0$
↑	1	0	1011	0	0	$A_3 = 0$ $A_4 = 1$	T_1	T_1	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b0$
↑	1	1	1100	0	0	$A_3 = 1$ $A_4 = 1$	T_1	T_2	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b0$

↑	1	1	1101	1	0	A ₃ = 1 A ₄ = 1	T ₂	T ₀	T ₁ → T ₂ $A \leftarrow A + 4'b0001$ $E \leftarrow 1'b1$
↑	1	0	1101	1	1	A ₃ = 1 A ₄ = 1	T ₀	T ₀	T ₂ → T ₀ $F \leftarrow 1'b1$
↑	1	0	1101	1	1	A ₃ = 1 A ₄ = 1	T ₀	T ₀	
	1	1	1101	1	1	A ₃ = 1 A ₄ = 1	T ₀	T ₁	
↑	1	1	0000	1	0	A ₃ = 0 A ₄ = 0	T ₁	T ₁	T ₀ → T ₁ $A \leftarrow 4'b0000$ $F \leftarrow 1'b0$
↑	1	1	0001	0	0	A ₃ = 0 A ₄ = 0	T ₁	T ₁	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b0$
↑	1	0	0010	0	0	A ₃ = 0 A ₄ = 0	T ₁	T ₁	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b0$
↑	1	0	0011	0	0	A ₃ = 0 A ₄ = 0	T ₁	T ₁	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b0$
↑	1	1	0100	0	0	A ₃ = 1 A ₄ = 0	T ₁	T ₁	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b0$
↑	1	1	0101	1	0	A ₃ = 1 A ₄ = 0	T ₁	T ₁	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b1$
	↓	0	0101	0	0	A ₃ = 1 A ₄ = 0	T ₀	T ₁	Asynchronous reset
↑	0	0	0101	0	0	A ₃ = 1 A ₄ = 0	T ₀	T ₁	pstate ≤ T ₀
↑	0	0	0101	0	0	A ₃ = 1 A ₄ = 0	T ₀	T ₁	pstate ≤ T ₀
	1	1	0101	0	0	A ₃ = 0 A ₄ = 0	T ₀	T ₁	
↑	1	1	0000	0	0	A ₃ = 0 A ₄ = 0	T ₁	T ₁	T ₀ → T ₁ $A \leftarrow 4'b0000$ $F \leftarrow 1'b0$
↑	1	1	0001	0	0	A ₃ = 0 A ₄ = 0	T ₁	T ₁	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b0$
↑	1	0	0010	0	0	A ₃ = 0 A ₄ = 0	T ₁	T ₁	$A \leftarrow A + 4'b0001$ $E \leftarrow 1'b0$
(이후 동작 같음)									