

Separate code to next_state and output from ASMD

```
module Sequential_Binary_Multiplier
    #(parameter dp_width = 5 parameter BC_size = 3) (
        output [2*dp_width-1:0] Product,
        output Ready,
        input [dp_width-1:0] Multiplicand, Multiplier,
        input Start, clock, reset_b
    );
    parameter S_idle = 3'b001, S_add = 3'b010, S_shift=3'b100;
    reg [2:0] state, next_state;
    reg [dp_width-1:0] A, B, Q; //Sized for datapath
    reg C;
    reg [BC_size-1:0] P;
    reg Load_regs, Decr_P, Add_regs, Shifth_regs;

    //Miscellaneous combinational logic
    assign Product = {A, Q};
    wire Zero = (P==0); // counter is zero
    wire Ready=(state == S_idle); // controller status

    //control unit
    always@(posedge clock, negedge reset_b)
        if(~reset_v) state <= S_idle;
        else state <= next_state;

    // next state logic
    always@(state, Start, Q[0], Zero) begin
        next_state <= S_idle;
        case(state)
            S_idle: if(Start) next_state <= S_add;
            S_add: next_state <= S_shift;
            S_shift:
                begin
                    if(Zero) next_state <= S_idle;
                    else next_state <= S_add;
                end
            default: next_state <= S_idle;
        endcase
    end
endmodule
```

```

end

// output logic
always@(state, Start, Q[0], Zero) begin
    Load_regs <= 0;
    Decr_P <= 0;
    Add_regs <= 0;
    Shift_regs <= 0;
    case(state)
        S_idle: if(Start) Load_regs <= 1;
        S_add:
            begin
                Decr_P <= 1;
                if(Q[0]) Add_regs <= 1;
            end
        S_shift:
            Shift_regs <= 1;
    end
end

//datapath unit
always@(posedge clock) begin
    if(Load_regs) begin
        P <= dp_width;
        A <= 0;
        C <= 0;
        B <= Multiplicand;
        Q <= Multiplier;
    end
    if(Add_regs) {C,A} <= A+ B;
    if(Shift_regs) {C,A,Q} <= ({C,A,Q} >> 1);
    if(Decr_P) P <= P-1;
end
endmodule

```

Design LD Driver


Design LD Driver with

- 1 12-bits binary counter I_Out (Predefined value of I_out is 2000)
- 1 structured module Counter_1E6
- 3 External input(main input) SW_ON, LD_ON, 12-bits I_set
- 2 12 bits Flip-Flop I_set_reg, I_incr
- 1 Flip-Flop LD_ON_reg
- 1 Master Clock 100MHZ (period = 10ns)

States

- initial state : S_0
- increase I_out : S_1
- decrease I_out : S_2
- keep I_out : S_3
- set high value from S_3 : S_4
- set low value from S_3 : S_5


Module Structure

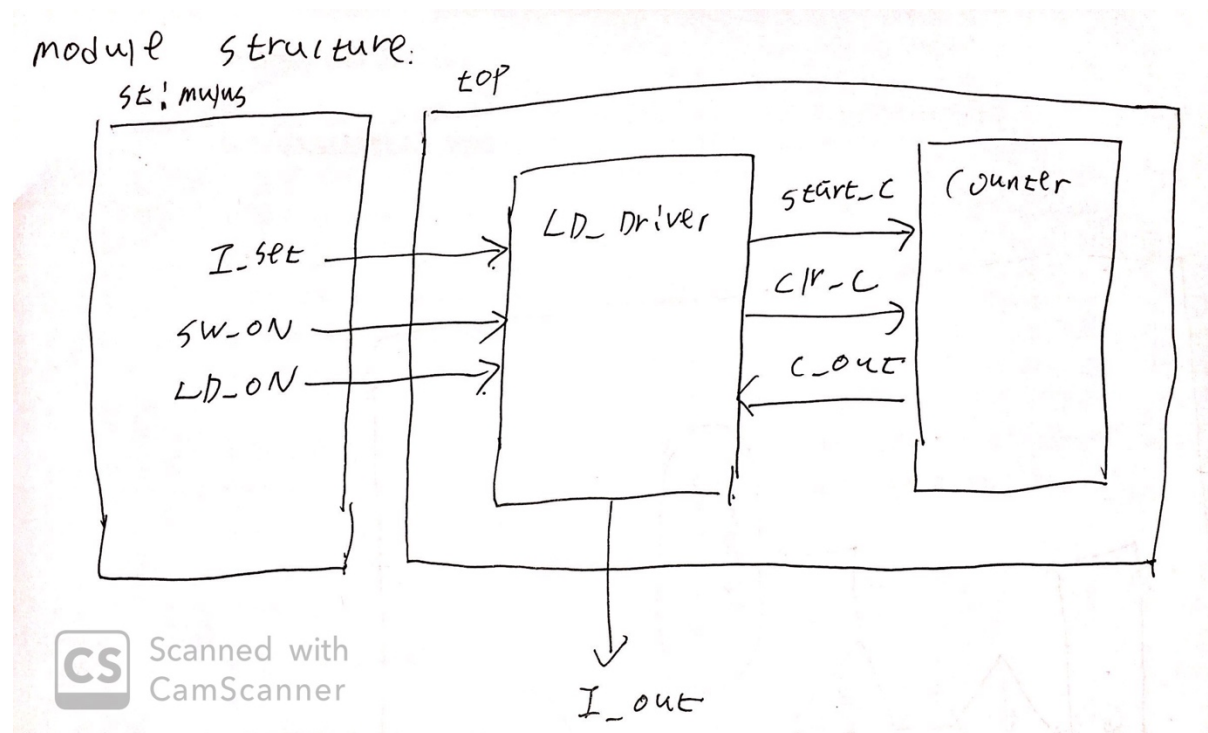

ASM Chart of Counter_1E6

ASM chart $S_0 = 2'b00$
 $S_1 = 2'b11$

Counter.

 

Scanned with
CamScanner

ASM Chart of LD_Driver

ASM chart

CLD - Driver.

All state

S0 = 3'b 000


S1 = 3'b 001

S2 = 3'b 010


S3 = 3'b 011

S4 = 3'b 100


S5 = 3'b 101

 


S0 initial state

 


S1 Increase I_{out}

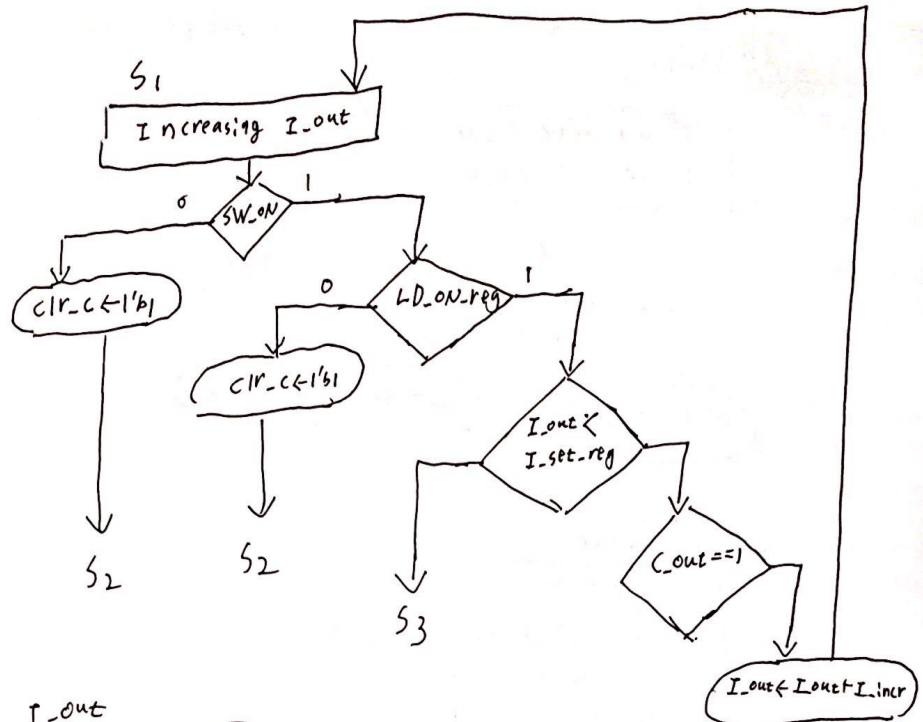


S2 Decrease I_{out}

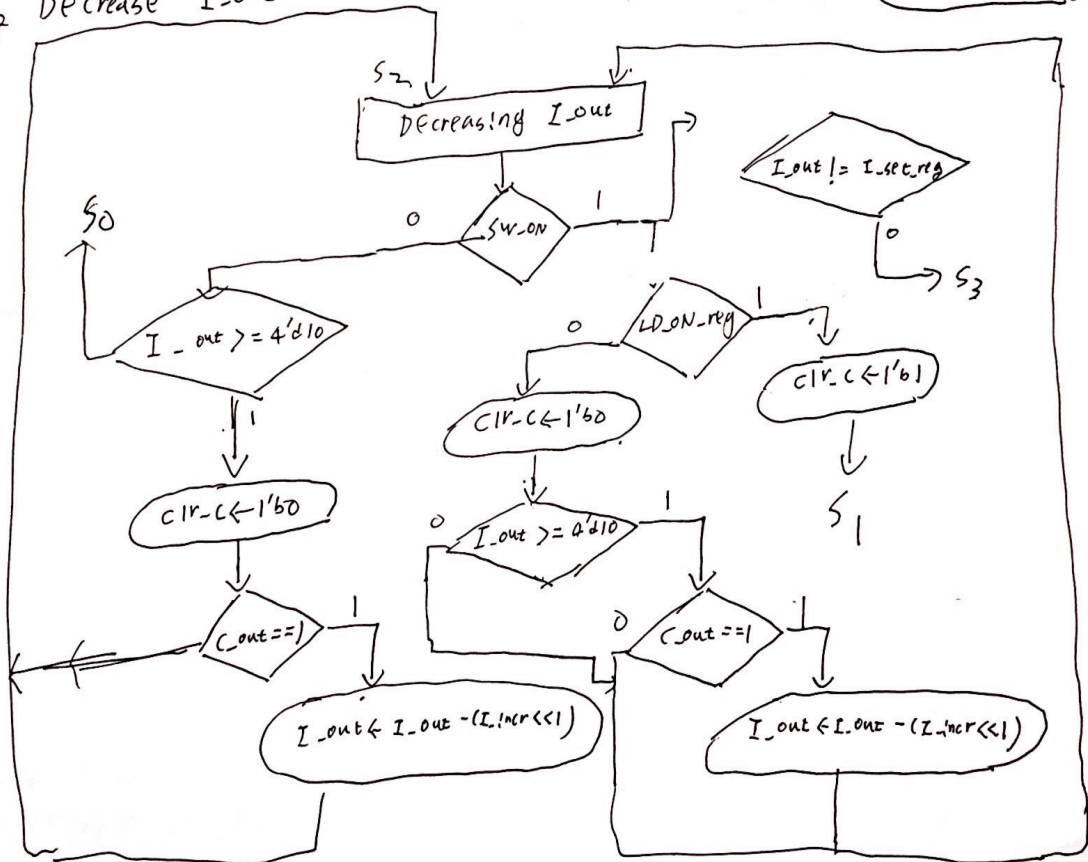


s_3 keeping I_out

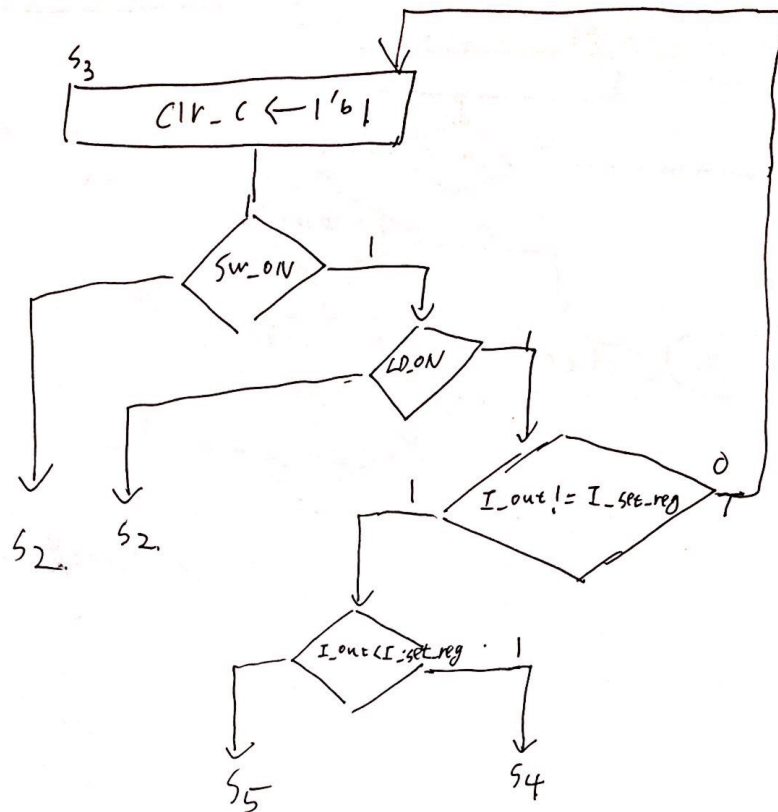

s_4 set high value from s_3

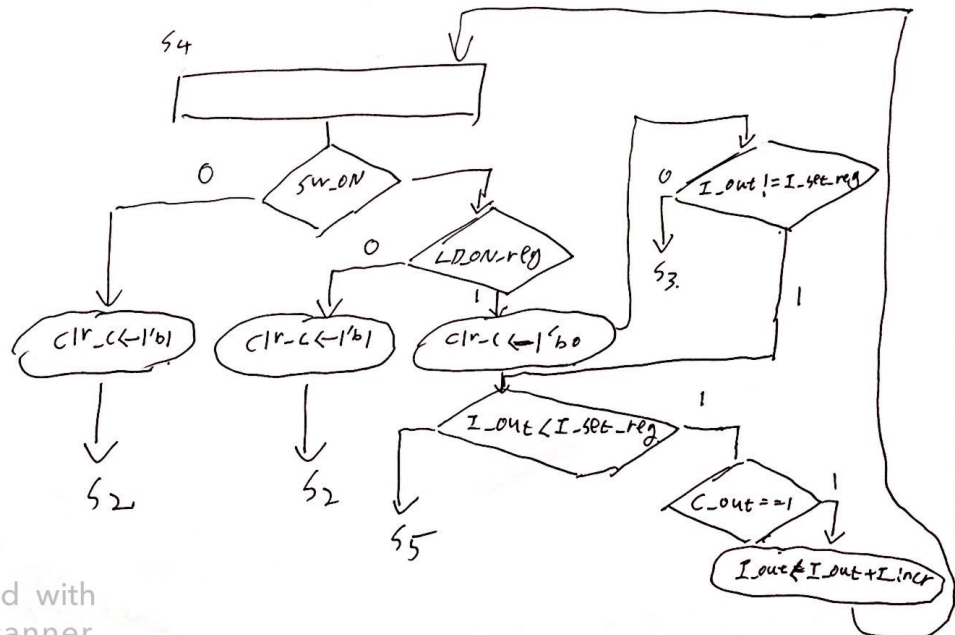

S₅ set low value from S₃

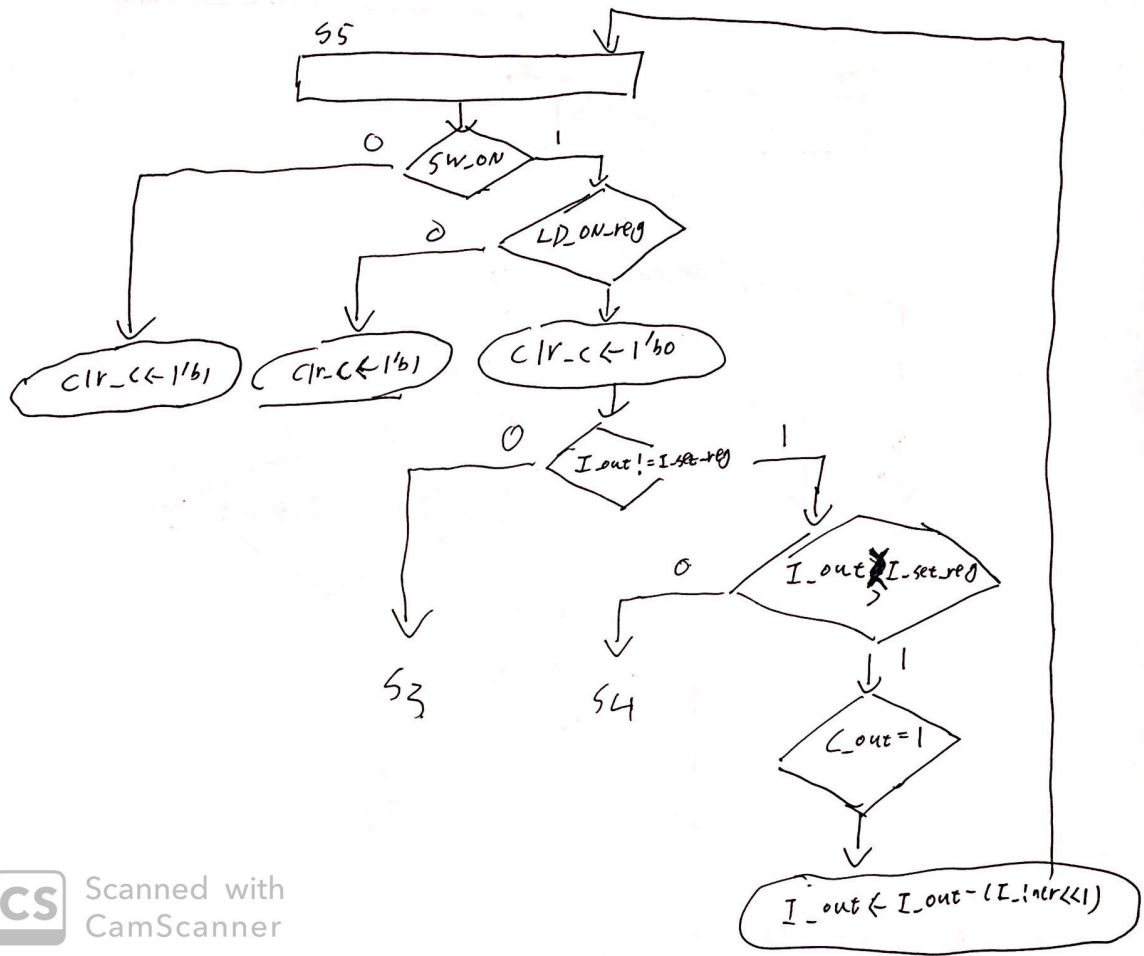

Verilog

top.v

```
module top(  
    output [12:0] I_out,  
    input [12:0] I_set,  
    input SW_ON, LD_ON,  
    input CLK, Clrn  
);  
    wire Start_C, Clr_C, C_out;  
  
    Counter_1E6_ASM_v_jin C1 (  
        .C_out(C_out),  
        .Start_C(Start_C),  
        .Clr_C(Clr_C),  
        .CLK(CLK),  
        .Clrn(Clrn));  
  
    LD_Driver_ASM_v_jin LD1 (  
        .I_out(I_out),  
        .Start_C(Start_C),  
        .Clr_C(Clr_C),  
        .I_set(I_set),  
        .SW_ON(SW_ON),  
        .LD_ON(LD_ON),  
        .C_out(C_out),  
        .CLK(CLK),  
        .Clrn(Clrn));  
endmodule
```

Counter_1E6_ASM_v_jin.v

```
module Counter_1E6_ASM_v_jin(
    output reg C_out,
    input Start_C, Clr_C,
    input CLK, Clrn
);

    reg [19:0] A; //Counter_1E6
    reg [1:0] pstate, nstate; // state
    //S0 : initial state, S1 : count
    parameter S0 = 2'b00, S1=2'b11;

    //state transition for control logic
    always @(posedge CLK, negedge Clrn) begin
        if(~Clrn) begin
            pstate <= S0;
            A <= 20'b0;
            C_out <= 1'b0;
        end
        else begin
            pstate <= nstate; //clocked operation
            //Register Transfer operation controlled by external input
            case(pstate)
                S0:
                    begin
                        if(Start_C) begin
                            A <= 20'b0;
                            C_out <= 1'b0;
                        end
                    end
                S1:
                    begin
                        if(Start_C) begin
                            if(Clr_C) begin
                                A <= 20'b0;
                                C_out <= 1'b0;
                            end
                        end
                    end
            endcase
        end
    end
endmodule
```

```

        end
        else begin
            if(A==20'd999999) begin
                A <= 20'b0;
                C_out <= 1'b1;
            end
            else begin
                A <= A + 1'b1;
                C_out <= 1'b0;
            end
        end
    end
end
end
endcase
end
end

// decide next state
always@(pstate, Start_C) begin
    case(pstate)
        S0:
            begin
                if(Start_C) nstate <= S1;
                else nstate <= S0;
            end
        S1:
            begin
                if(Start_C) nstate <= S1;
                else nstate <= S0;
            end
    endcase
end
end
endmodule

```

LD_Driver_ASM_v_jin.v

```
module LD_Driver_ASM_v_jin(
    output reg [12:0] I_out,
    output reg Start_C,
    output reg Clr_C,
    input [12:0] I_set,
    input SW_ON, LD_ON, C_out,
    input CLK, Clrn
);
    reg LD_ON_reg; // store LD_ON
    reg [12:0] I_set_reg; //store i_set value
    reg [12:0] I_incr; // setting incremental
    reg [2:0] pstate, nstate;

    //Encode the states
    parameter S0=3'b000, S1=3'b001, S2=3'b010, S3=3'b011, S4=3'b100,
    S5=3'b101;

    //state transition
    always @(posedge CLK, negedge Clrn) begin
        if(~Clrn) begin
            pstate <= S0;
            I_out <= 13'b0;
            Start_C <= 1'b0;
            Clr_C <= 1'b0;
            LD_ON_reg <= 1'b0;
            I_set_reg <= 13'b0;
            I_incr <= 13'b0;
        end
        else begin
            pstate <= nstate; //clocked operation
            // if SW_ON == 0, set LD_ON_reg 1'b0
            if(SW_ON) LD_ON_reg <= LD_ON;
            else LD_ON_reg <= 1'b0;
            // store i_set
            I_set_reg <= I_set;
        end
    end
endmodule
```

```

// make incr
I_incr <= (I_set >> 10); // divide by 1024(approx 1000)

//Register Transter operation
case(pstate)
  S0:
  begin
    I_out <= 13'b0;
    if(SW_ON) begin
      Start_C <= 1'b1;
      Clr_C <= 1'b0;
    end
    else Start_C <= 1'b0;

  end
  S1:
  begin
    if(SW_ON) begin
      if(LD_ON_reg) begin
        Clr_C <= 1'b0;
        if(I_out < I_set_reg) begin
          if(C_out == 1'b1) begin
            I_out <= I_out+ I_incr;
          end
        end
      end
    end
    else Clr_C <= 1'b1;
  end
  S2:
  begin
    if(SW_ON) begin
      if(!LD_ON_reg) begin
        Clr_C <= 1'b0;
        if(I_out >= 4'b1010) begin

```

```

        if(C_out == 1'b1) begin
            //multiple by 2
            L_out <= L_out-(L_incr << 1);
        end
    end
end
else Clr_C <= 1'b1;
end
else begin
    if(L_out >= 4'b1010) begin
        Clr_C <= 1'b0;
        if(C_out == 1'b1) begin
            L_out <= L_out-(L_incr << 1);
        end
    end
    else Clr_C <= 1'b1;
end
end
S3:
begin
    Clr_C <= 1'b1;
end

S4:
begin
    if(SW_ON) begin
        if(LD_ON_reg) begin
            Clr_C <= 1'b0;
            if(L_out < L_set_reg) begin
                if(C_out == 1'b1) begin
                    L_out <= L_out+ L_incr;
                end
            end
        end
        else Clr_C <= 1'b1;
    end
    else Clr_C <= 1'b1;
end

```

```

        end

        S5:
        begin
            if(SW_ON) begin
                if(LD_ON_reg) begin
                    Clr_C <= 1'b0;
                    if(I_out > I_set_reg) begin
                        if(C_out == 1'b1) begin
                            I_out <= I_out-(I_incr<<1);
                        end
                    end
                end
            end
            else Clr_C <= 1'b1;
        end
    end

endcase
end
end

always @(SW_ON, LD_ON_reg, pstate, I_out, I_set_reg) begin
    case(pstate)
        S0:
        begin
            if(SW_ON & LD_ON_reg) nstate <= S1;
            else nstate <= S0;
        end

        S1:
        begin
            if(SW_ON & LD_ON_reg) begin
                if(I_out >= I_set_reg) nstate <= S3;
                else nstate <= S1;
            end
            else nstate <= S2;
        end
    end
end

```

```

end

S2:
begin
    if(SW_ON) begin

        if(LD_ON_reg) nstate <= S1;
        else nstate <= S2;
    end
    else
        if(I_out <= 4'b1010) nstate <= S0;
        else nstate <= S2;
    end

default:
begin
    if(SW_ON & LD_ON_reg) begin
        if (I_out != I_set_reg) begin
            if(I_out < I_set_reg) nstate <= S4; //i_set incr
            else nstate <= S5;
        end
        else nstate <= S3;
    end
    else nstate <= S2;
end
endcase
end
endmodule

```


sti.v

```
`timescale 1ns/1ns
module sti;

    reg CLK, Clrn;
    reg [12:0] L_set;
    wire [12:0] L_out;
    reg SW_ON, LD_ON;

    //set end time
    initial begin
        #40E6 $finish;
    end


    initial
    begin
        CLK <= 1'b0;
        Clrn <= 1'b0;
        SW_ON <= 1'b1;
        LD_ON <= 1'b1;
        L_set <= 13'd1024;
        #20 Clrn <= 1'b1; // reset two clock edge
        #5E6 L_set <= 13'd2048;
        #2E6 L_set <= 13'd1024;
        #4E6 L_set <= 13'd2048;
        #8E6 L_set <= 13'd1024;
        #6E6 LD_ON <= 1'b0; //start decreasing
        #3E6 L_set <= 13'd2048;
        #2E6 L_set <= 13'd1024;
        #2E6 LD_ON <= 1'b1; //again start increasing
        #2E6 SW_ON <= 1'b0; //turn off the switch
        #1E6 SW_ON <= 1'b1; //again switch on
    end

    always #5 CLK <= ~CLK; //clock generator
```

```
top t1 (  
    .I_out(I_out),  
    .I_set(I_set),  
    .SW_ON(SW_ON),  
    .LD_ON(LD_ON),  
    .CLK(CLK),  
    .Clrn(Clrn));  
  
always @(I_out) begin  
    $monitor("I_out = %d, time = %0d", I_out, $time);  
end  
endmodule
```


RTL Simulation

1) Increasing I_out

 

SW_ON = 1
LD_ON = 1
LD_ON_reg = 1
I_set = 1024
I_incr = 1
State : S1 (001)

2) change I_set during increasing I_out

 

SW_ON = 1
LD_ON = 1
LD_ON_reg = 1
I_set = 2048
I_incr = 2
State : S1 (001)

3) change again I_{set} during increasing I_{out}

CLK	1					
Clrn	1					
I_{set}	2048	2048		1024		
I_{incr}	2	2		1		
C_{out}	0					
I_{out}	887	897	899	900	901	
SW_ON	1					
LD_ON	1					
pstate	001	001				
nstate	001	001				
Counter						
A	142					
Start_C	1					
Clr_C	0					


SW_ON = 1
LD_ON = 1
LD_ON_reg = 1
 I_{set} = 1024
 I_{incr} = 1
State : S1 (001)

4) reach I_{set} value

CLK	0					
Clrn	1					
I_{set}	1024	1024				
I_{incr}	1	1				
C_{out}	0					
I_{out}	1024	1022	1023	1024		
SW_ON	1					
LD_ON	1					
pstate	011	001		011		
nstate	011	001		011		
Counter						
A	0			0		
Start_C	1					
Clr_C	1					


SW_ON = 1
LD_ON = 1
LD_ON_reg = 1
 I_{set} = 1024
 I_{incr} = 1
State : S3 (011)

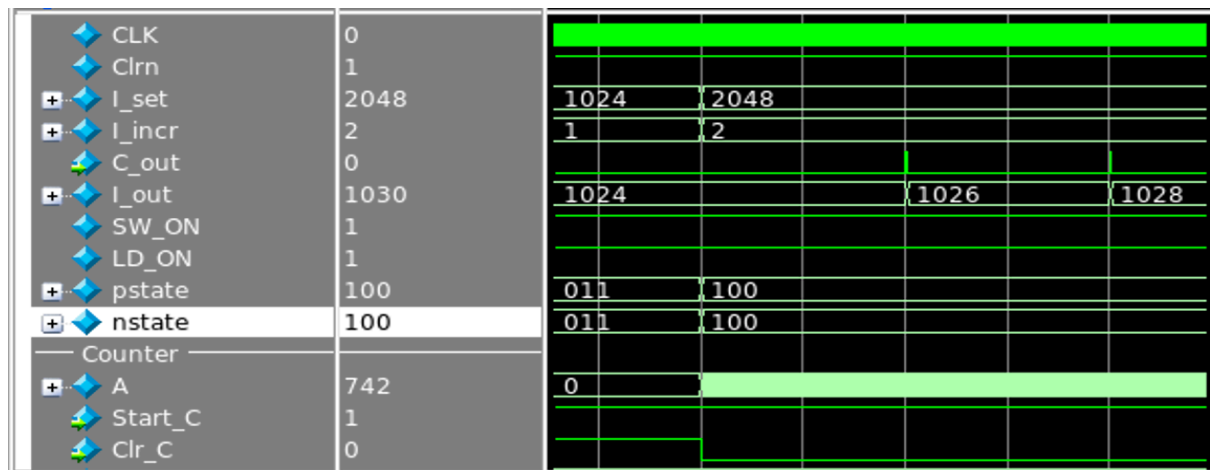5) change High value of I_set when keep I_out




SW_ON = 1
 LD_ON = 1
 LD_ON_reg = 1
 I_set = 2048
 I_incr = 2
 State : S4 (100)

6) reach High value of I_set

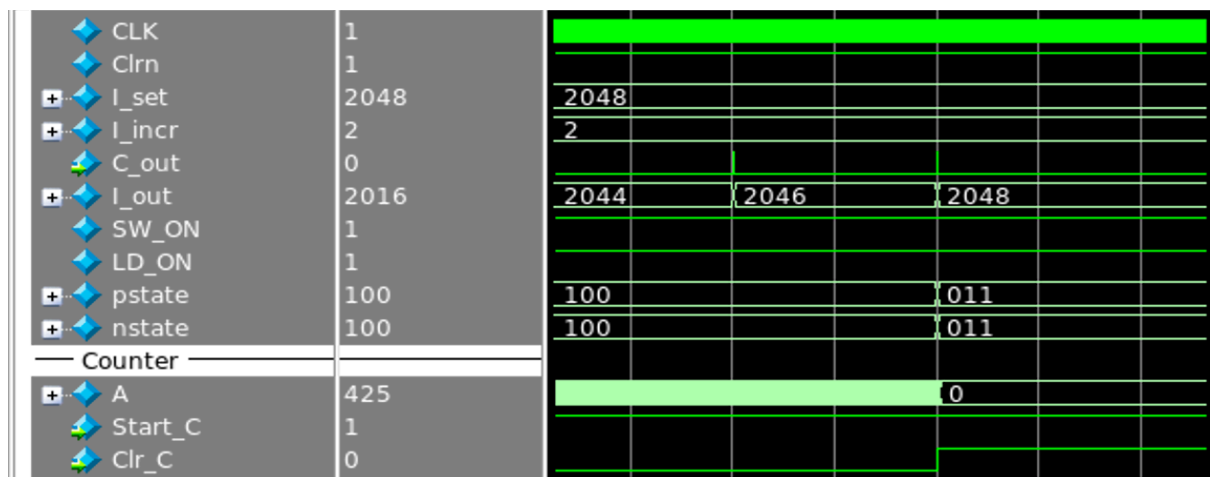

SW_ON = 1
 LD_ON = 1
 LD_ON_reg = 1
 I_set = 2048
 I_incr = 2
 State : S3 (011)

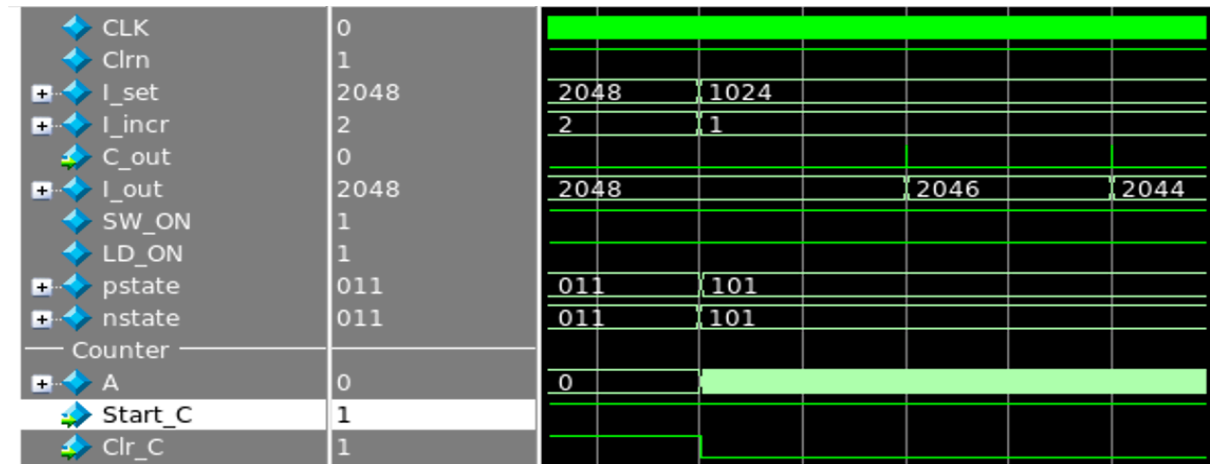7) change low value of I_set when keep I_out



SW_ON = 1

LD_ON = 1


LD_ON_reg = 1

I_set = 1024

I_incr = 1 (I_decr : 2)

State : S5 (101)

8) Decreasing I_out when LD_ON is 0

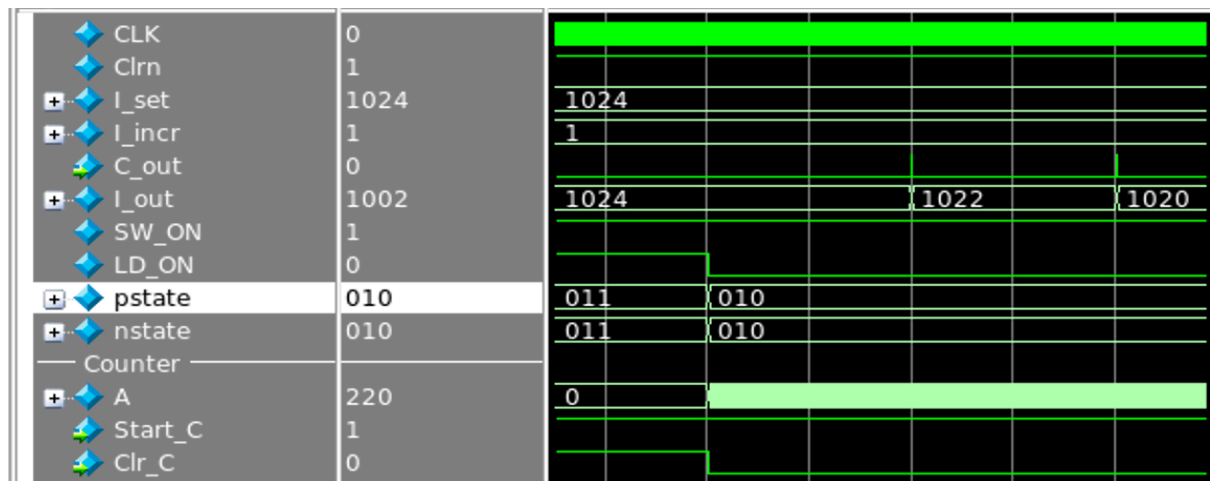

SW_ON = 1

LD_ON = 0


LD_ON_reg = 0

I_set = 1024

I_incr = 1 (I_decr : 2)

State : S2 (010)

9) change I_set during decreasing I_out

 

SW_ON = 1

LD_ON = 0


LD_ON_reg = 0

I_set = 2048

I_incr = 2 (I_decr : 4)

State : S2 (010)

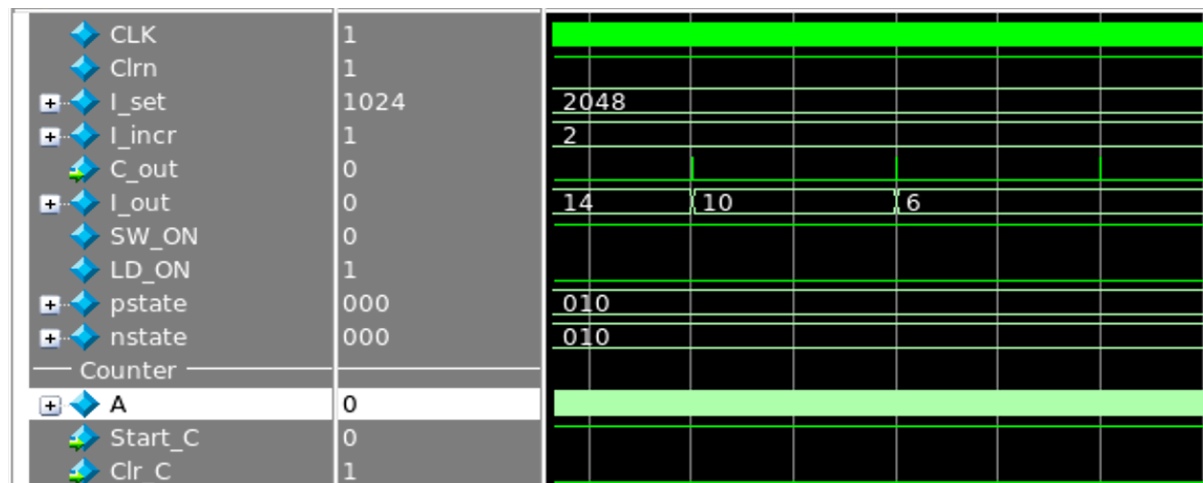10) keep I_out below 10 and stay in switch on



SW_ON = 1

LD_ON = 0


LD_ON_reg = 0

I_set = 2048

I_incr = 2 (I_decr : 4)

State : S2 (010)

11) change LD_ON to 1

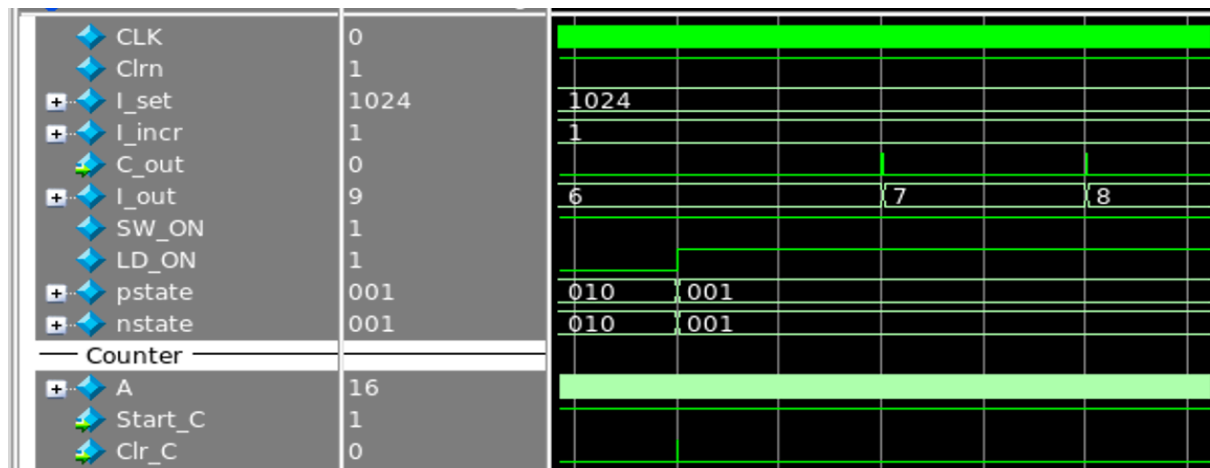

SW_ON = 1

LD_ON = 1


LD_ON_reg = 1

I_set = 1024

I_incr = 1 (I_decr : 2)

State : S1 (001)

12) Switch off

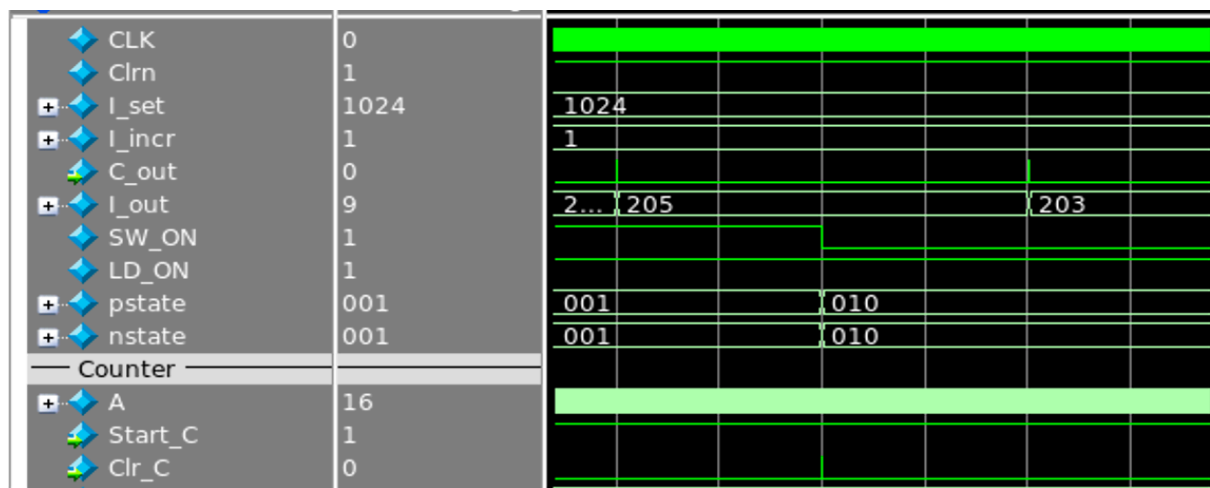

SW_ON = 0

LD_ON = 1


LD_ON_reg = 0

I_set = 1024

I_incr = 1 (I_decr : 2)

State : S2 (010)

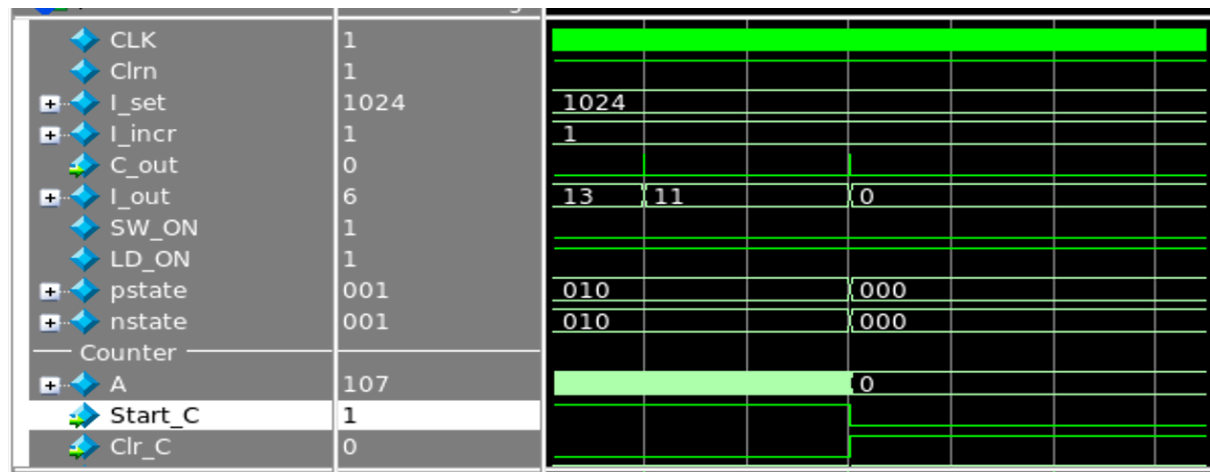13) When I_out reaches below 10, initialize I_out to 0 and go to initial state



SW_ON = 0

LD_ON = 1


LD_ON_reg = 0

I_set = 1024

I_incr = 1 (I_decr : 2)

State : S0 (000)

14) Switch on again

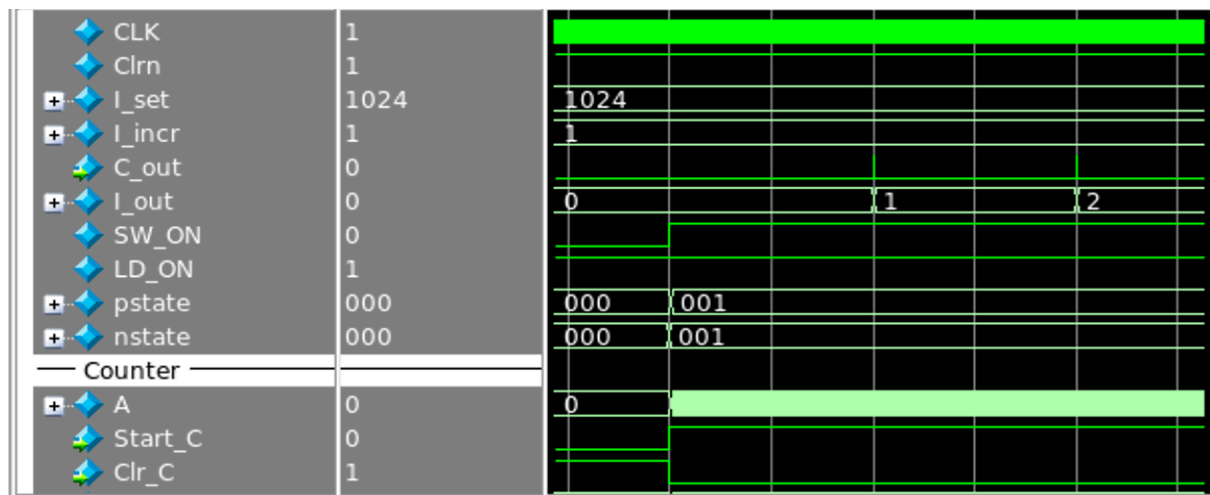

SW_ON = 1

LD_ON = 1

LD_ON_reg = 1

I_set = 1024

I_incr = 1

State : S1 (001)